



非常天空

Computer Organization & Design

Hardware/Software interface

楼学庆

浙江大学计算机学院

<http://10.214.47.99/>

[Email:hzlou@163.com](mailto:hzlou@163.com)



玉泉校区曹光彪东楼507室



12:53:00

浙江大学计算机学院

联系方式

- 网站:
 - <http://10.214.47.99>
- 邮箱:
 - hzlou@163.com (不收作业)



九·一八事变76周年

- 抗日战争的开始
 - 从1931年9月18日，日本关东军完成了向中国军队进攻，向中国百姓动武的最后准备，悍然发动了震惊中外的“九一八”事变。





Computer Organization & Design

第04章: Datapath & Control

楼学庆

<http://10.214.47.99/>

[Email:hzlou@163.com](mailto:hzlou@163.com)



玉泉校区曹光彪东楼507室




12:53:00

浙江大学计算机学院

Chapter 4

■ Topics: Datapath & Control

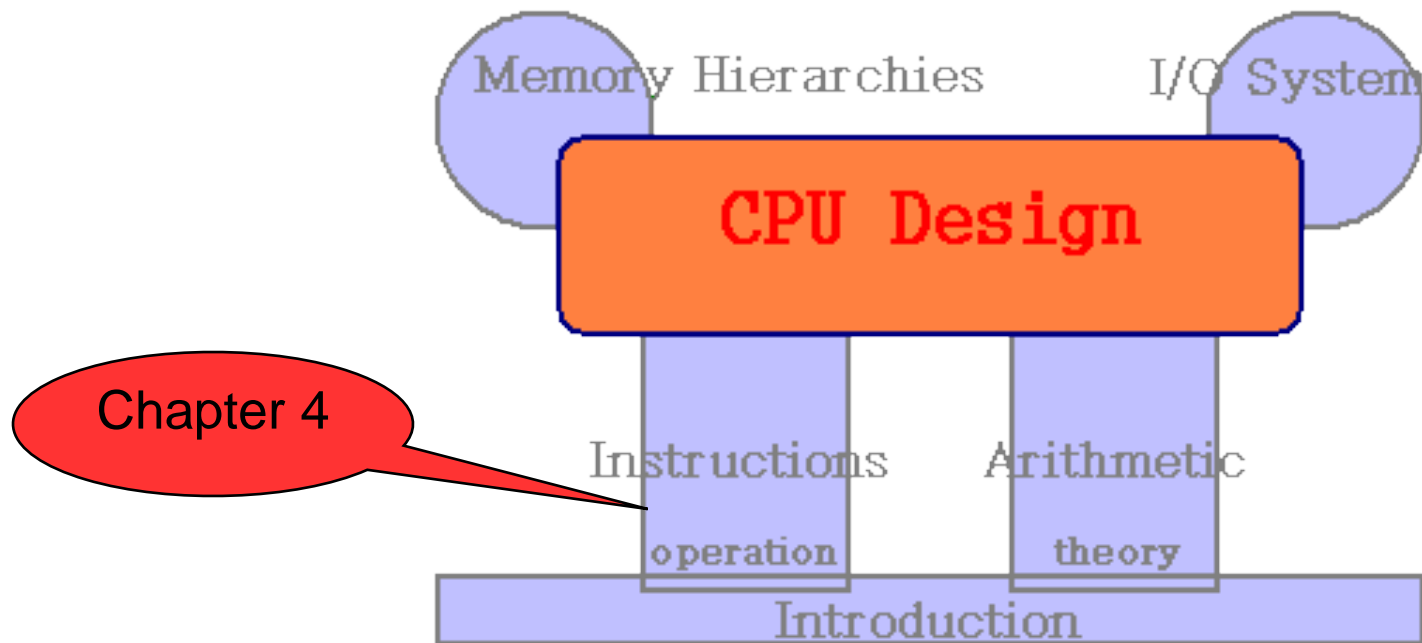



12:53:00

浙江大学计算机学院




The Processor: Datapath & Control

- We're ready to look at an implementation of the MIPS
- Simplified to contain only:
 - memory-reference instructions: lw, sw
 - arithmetic-logical instructions: add, sub, and, or, slt
 - control flow instructions: beq, j
- Generic Implementation:
 - use the program counter (PC) to supply instruction address
 - get the instruction from memory
 - read registers
 - use the instruction to decide exactly what to do




State Elements

 - Unclocked vs. Clocked
- Clocks used in synchronous logic
 - when should an element that contains state be updated?



Our Implementation

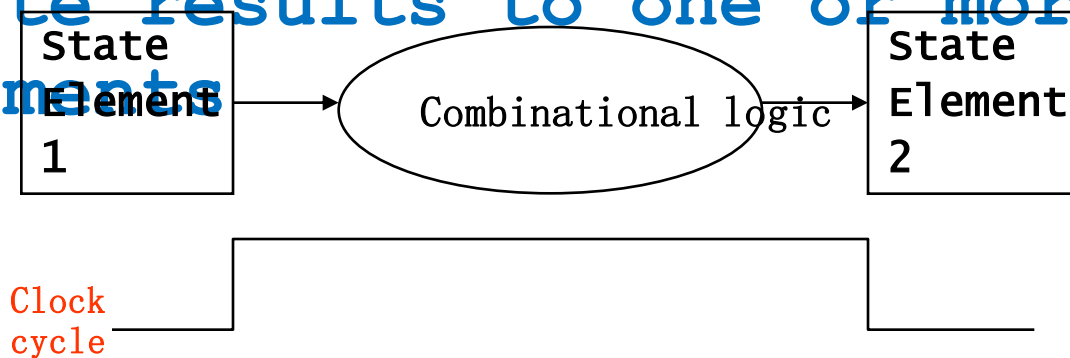- An edge triggered methodology
- Typical execution:
 - read contents of some state elements,
 - send values through some combinational logic
 - write results to one or more state elements






Basic elements

Basic logic gate.

- AND: $S=A \cdot B$
- OR : $S=A+B$
- NOT: $S=\sim A$

A	B	$A \cdot B$	$A+B$	$\sim A$
0	0	0	0	1
0	1	0	1	1
1	0	0	1	0
1	1	1	1	0

 
 
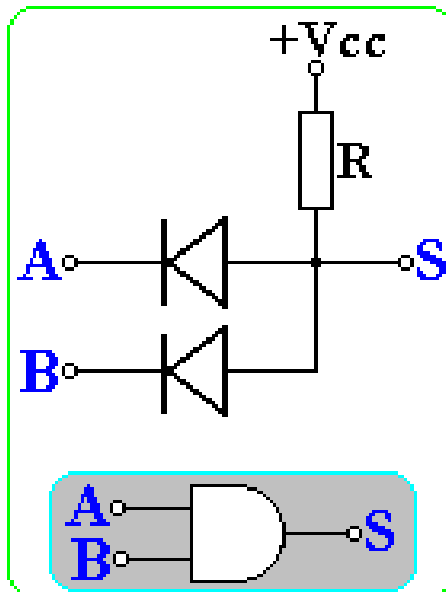


MUX

- 多路开关：有若干个输入，由控制端决定那一路输入将输出。

□ 经常具有多路并行

C	S
0	A
1	B

   

Adder

■ Half adder:


A	0	0	1	1
B	0	1	0	1
S	0	1	1	0

■ Full adder: $S=A+B$

□ Input: A, B, C₀. Output: Sum,




□ $S = A \oplus B \oplus C$

A	0	0	1	1	0	1	1
B	0	1	0	1	0	1	1
C	0	0	0	0	1	1	1
S	0	1	1	0	1	0	1
C ₊₁	0	0	0	1	0	1	1

 


串行进位加法器

   - 4位串行进位加法器： $S=A+B$
 - 各位串行进行。
 - 同时根据结果产生各种标记状态。



Adder

■ 32-bit Adder

 



ALU

■ 算术逻辑运算器ALU：即运算

□ 5 Operations

□ "Set on less than":
if $A < B$ then Result=1;
else Result=0.

Operation	Function
000	And
001	Or
010	Add
110	Sub
111	Slt

 
 


ALU Control

■ ALU Control:

- **ALU由ALUcontrol控制:**
ALUcontrol由ALUop和指令的低6位(5-0)联合产生ALU控制码。
- 这样的好处在于分级控制, 对于用的最多的加、减操作, 系统只需给出两位的ALUop即可。


ALUop	Operation	Function
10	000	And
10	001	Or
00	010	Add
01	110	Sub
10	111	Slt

 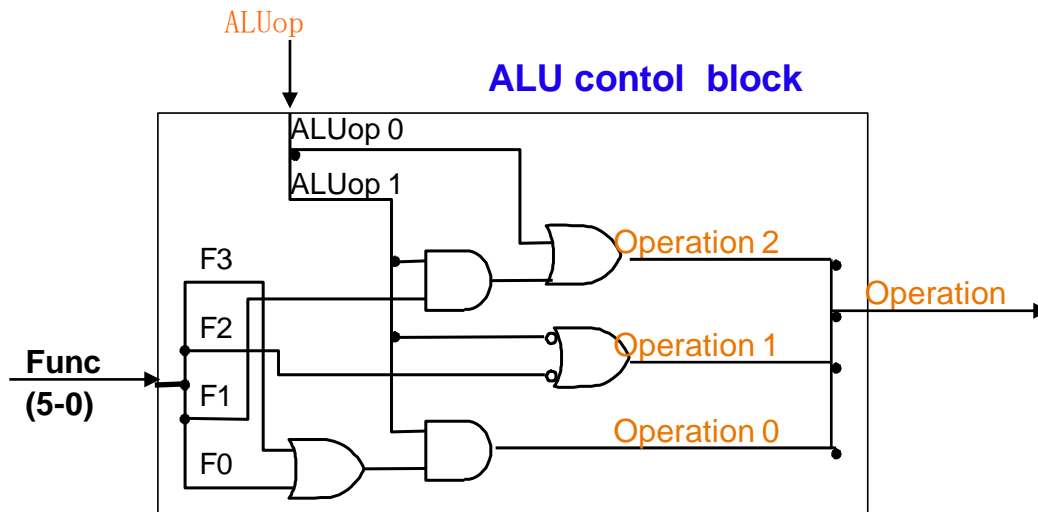

ALU Control

■ ALUop与Func联合对ALU的控制



ALUOp		Func field						Operation	ALU Function
ALUOp1	ALUOp0	F5	F4	F3	F2	F1	F0		
0	0	X	X	X	X	X	X	010	Add
1	1	X	X	X	X	X	X	110	Sub
1	X	X	X	0	0	0	0	010	Add
1	X	X	X	0	0	1	0	110	Sub
1	X	X	X	0	1	0	0	000	And
1	X	X	X	0	1	0	1	001	Or
1	X	X	X	1	0	1	0	111	SetonLT

 

ALU Control

■ ALU控制:

 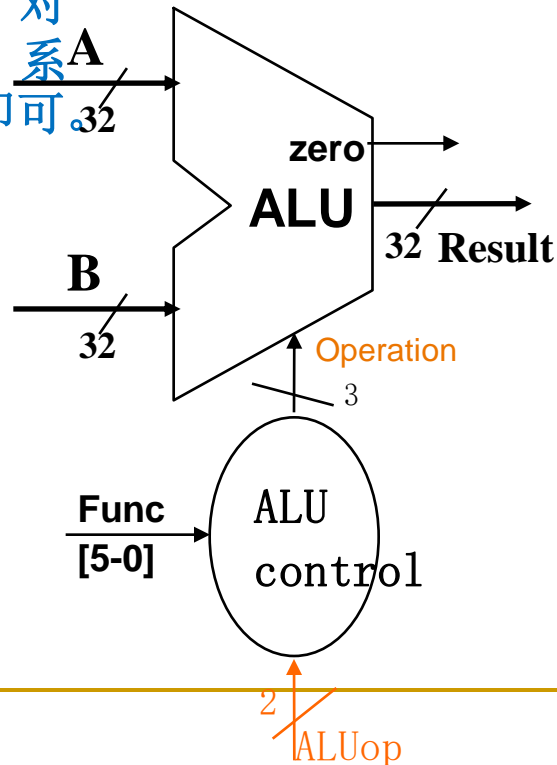
- ALU由ALUcontrol控制:
ALUcontrol由ALUop和指令的低6位(5-0)联合产生ALU控制码。
- 这样的好处在于分级控制, 对于用的最多的加、减操作, 系统只需给出两位的ALUop即可



REGISTER

■ Register

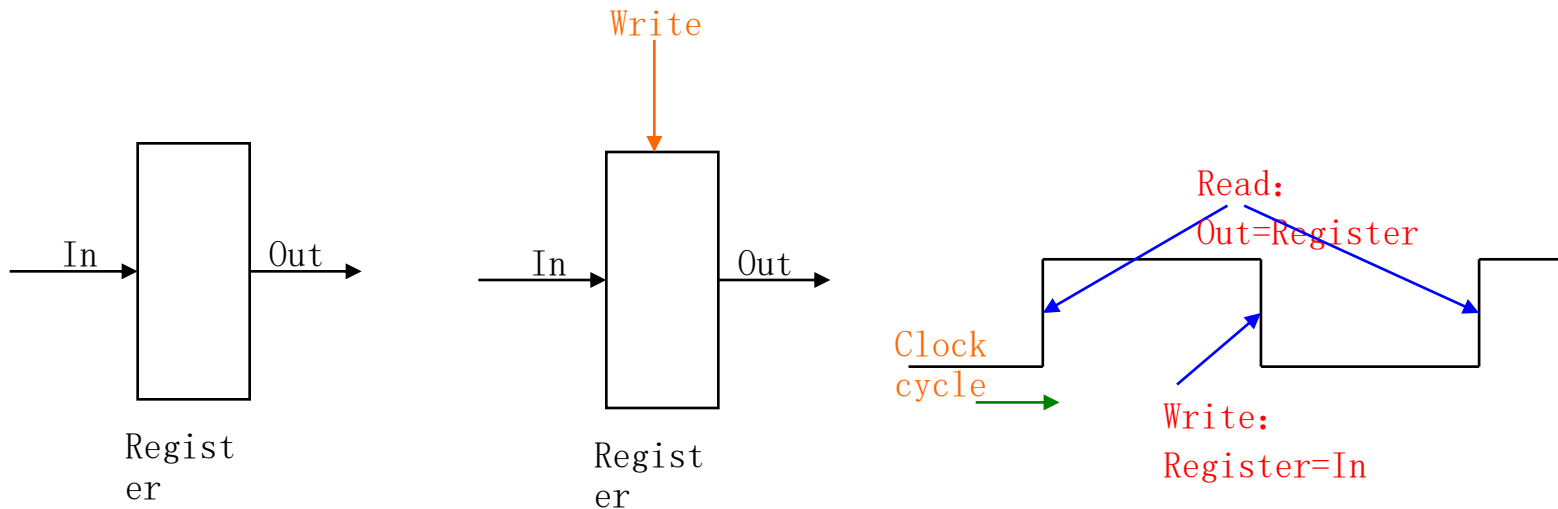
- State element.
- Can be controlled by **Write** signal.



Memory

■ 存储器:

 
- 可分为指令存储器与数据存储器;
- 指令存储器设为只读; 输入指令地址, 输出指令。
- 数据存储器可以读写, 由MemRead和MemWrite控制。按地址读出数据输入, 或将写数据写入地址所指存储器单元。



Register File


■ Register File:

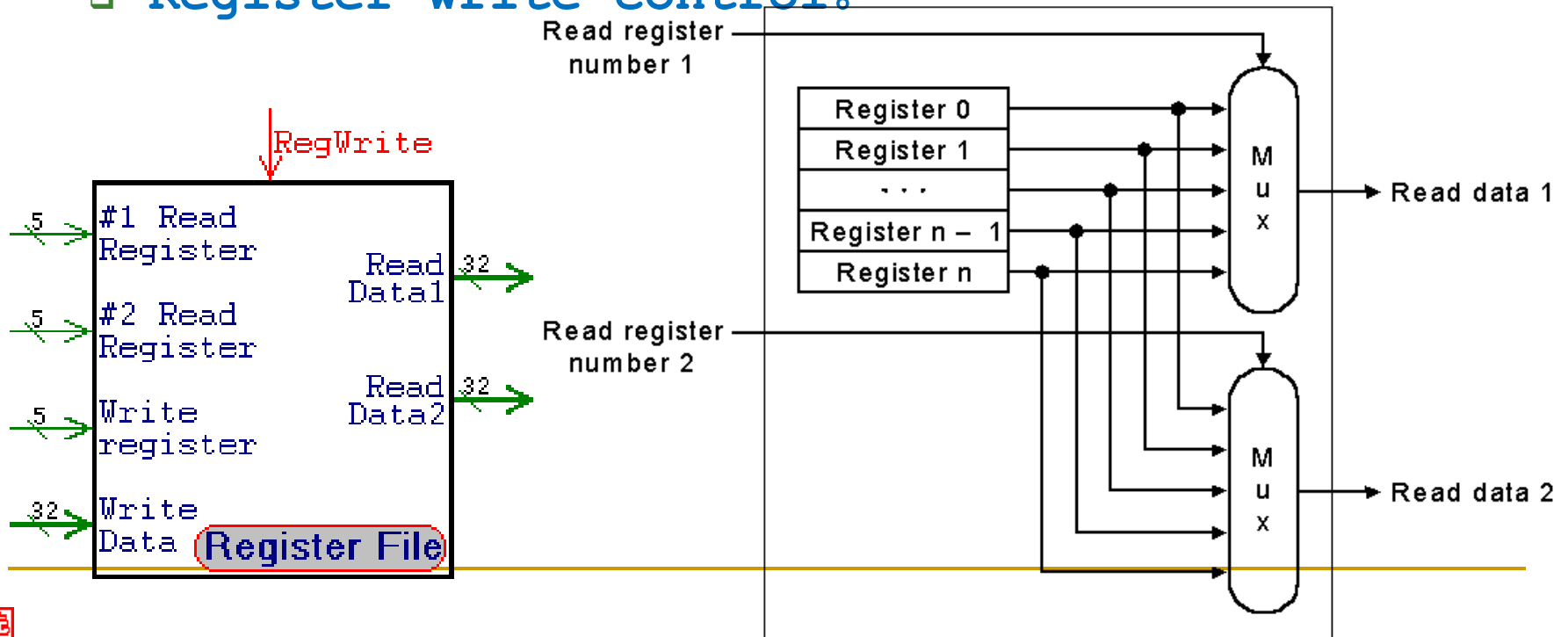- 32 32-bit Registers;
- Input: 2 32-bit;
- Output: 32-bit data, 32-bit register number;
- Register write control.



Register File

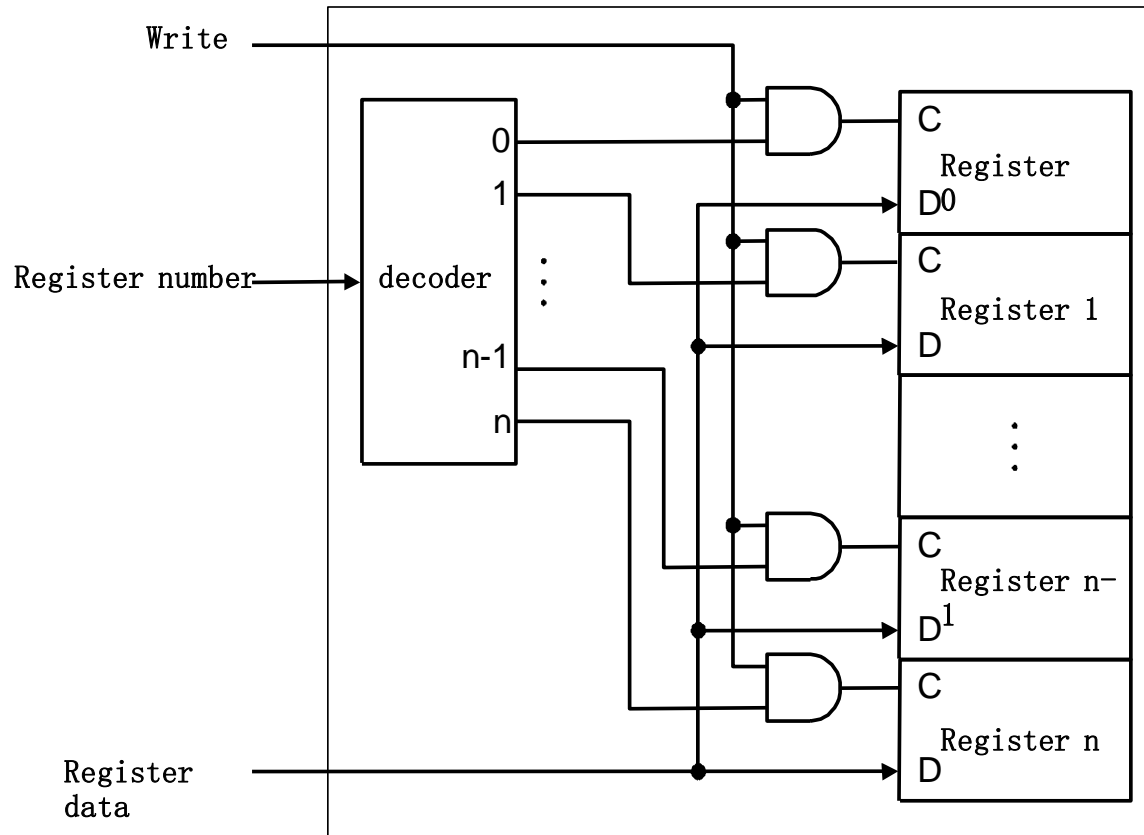- 写寄存器: we still use the real clock to determine when to write



32个Register的功用

- 寄存器组有32个32位寄存器，其功用分配如下表：

Name	Register number	Usage
\$zero	0	the constant value 0
\$at	1	reserved for the assembler
\$v0-\$v1	2-3	values for results and expression evaluation
\$a0-\$a3	4-7	arguments
\$t0-\$t7	8-15	temporaries
\$s0-\$s7	16-23	saved
\$t8-\$t9	24-25	more temporaries
\$k0-\$k1	26-27	reserved for the operating system
\$gp	28	global pointer
\$sp	29	stack pointer
\$fp	30	frame pointer
\$ra	31	return address


The other elements

■ Sign Extend:

- 将16位的补码表示的有符号立即数，扩展为32位。
- 方法：只需重复符号位即可。


■ Shift:

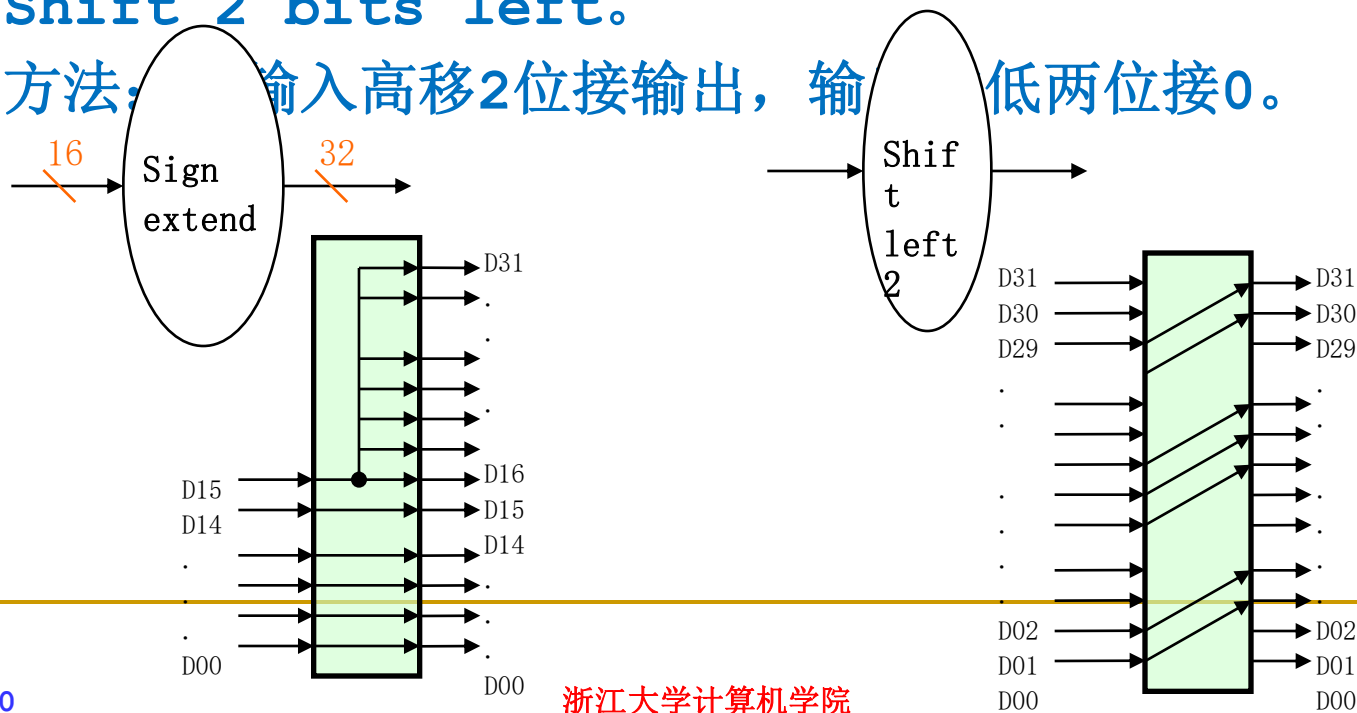- Shift 2 bits left.
- 方法：输入高移2位接输出，输入低两位接0。



Simple Implementation

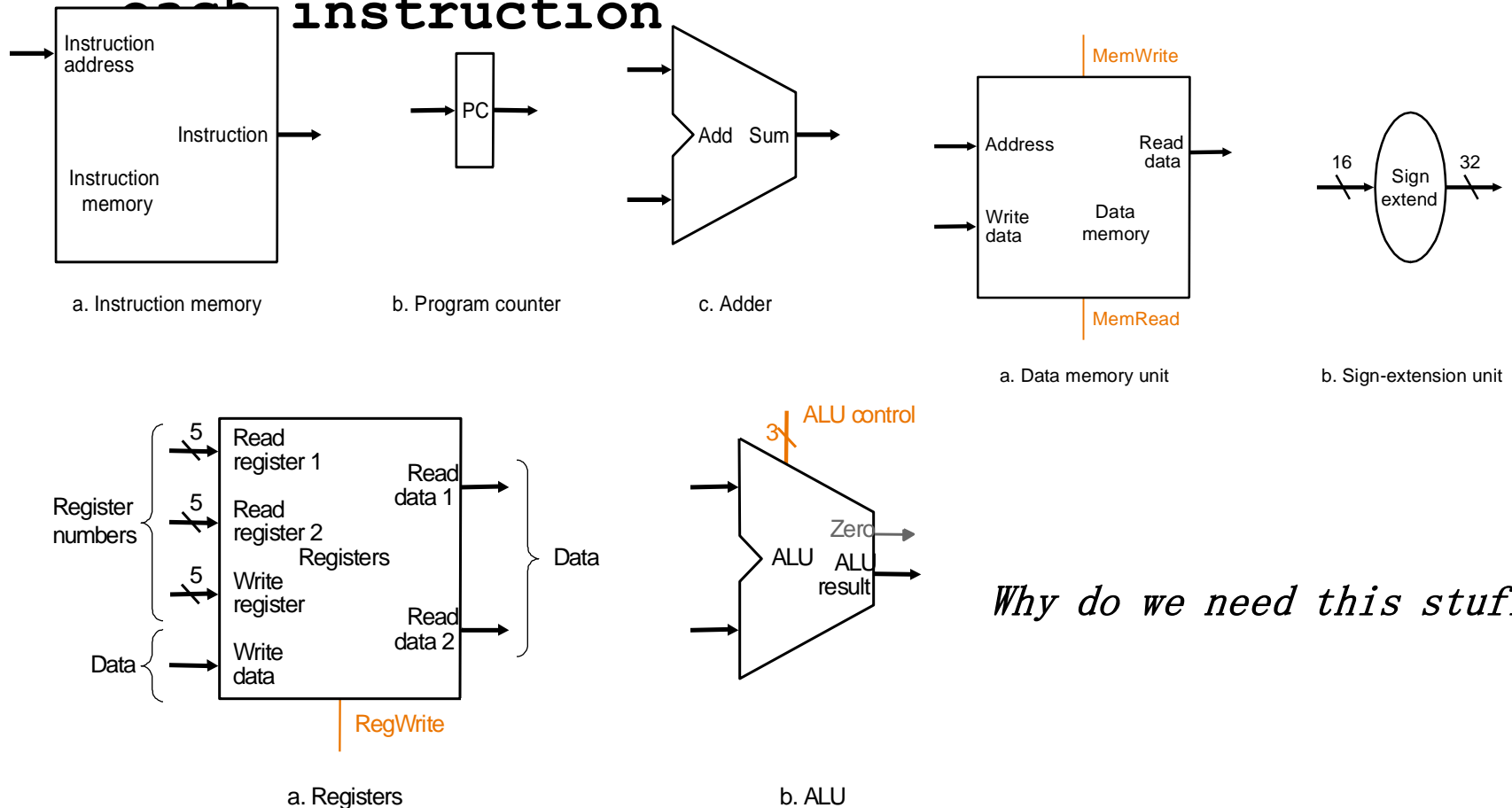- Include the functional units we need for each instruction




Why do we need this stuff?

Section 2


datapath

Building a

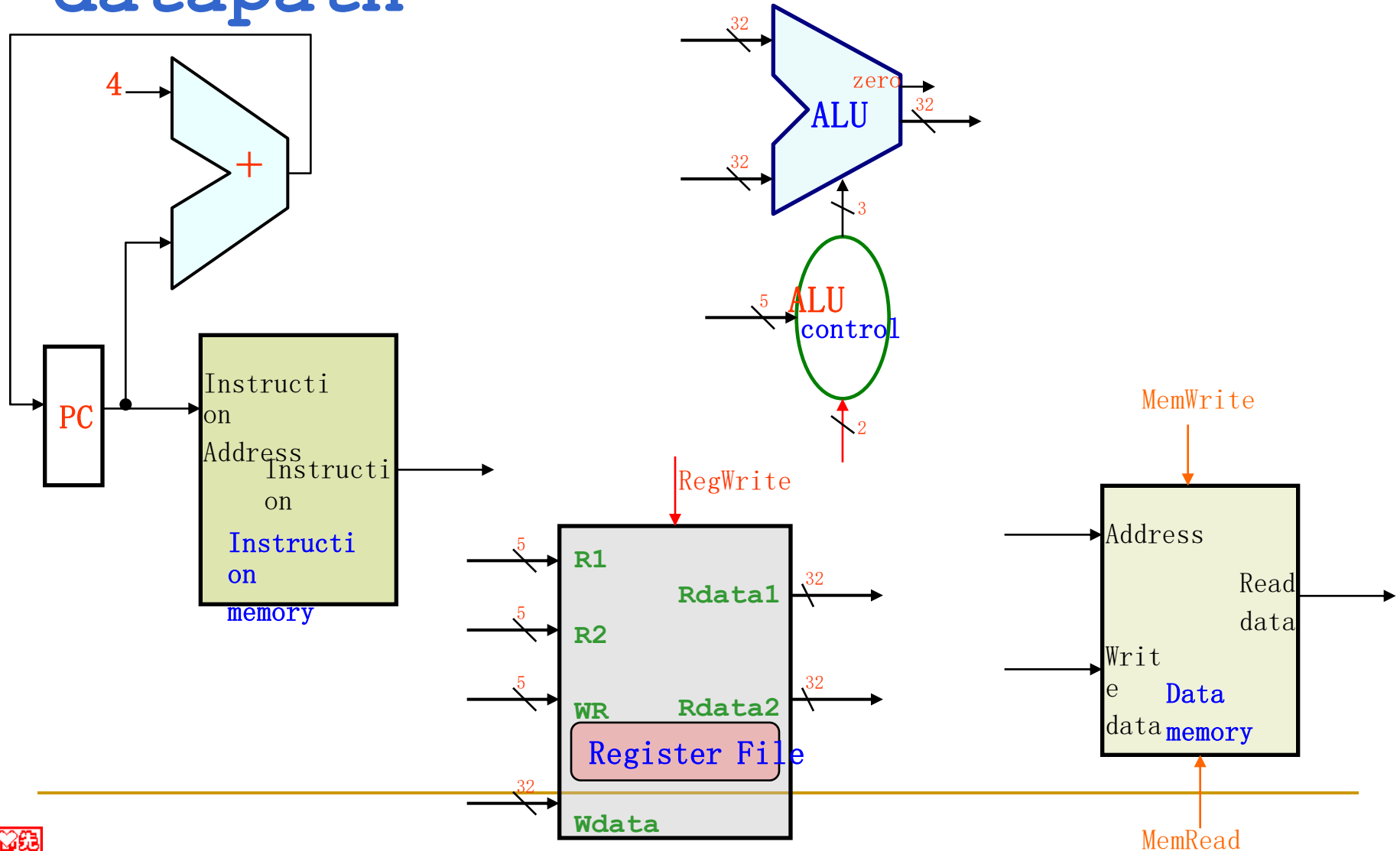

More Implementation

■ Abstract / Simplified View:


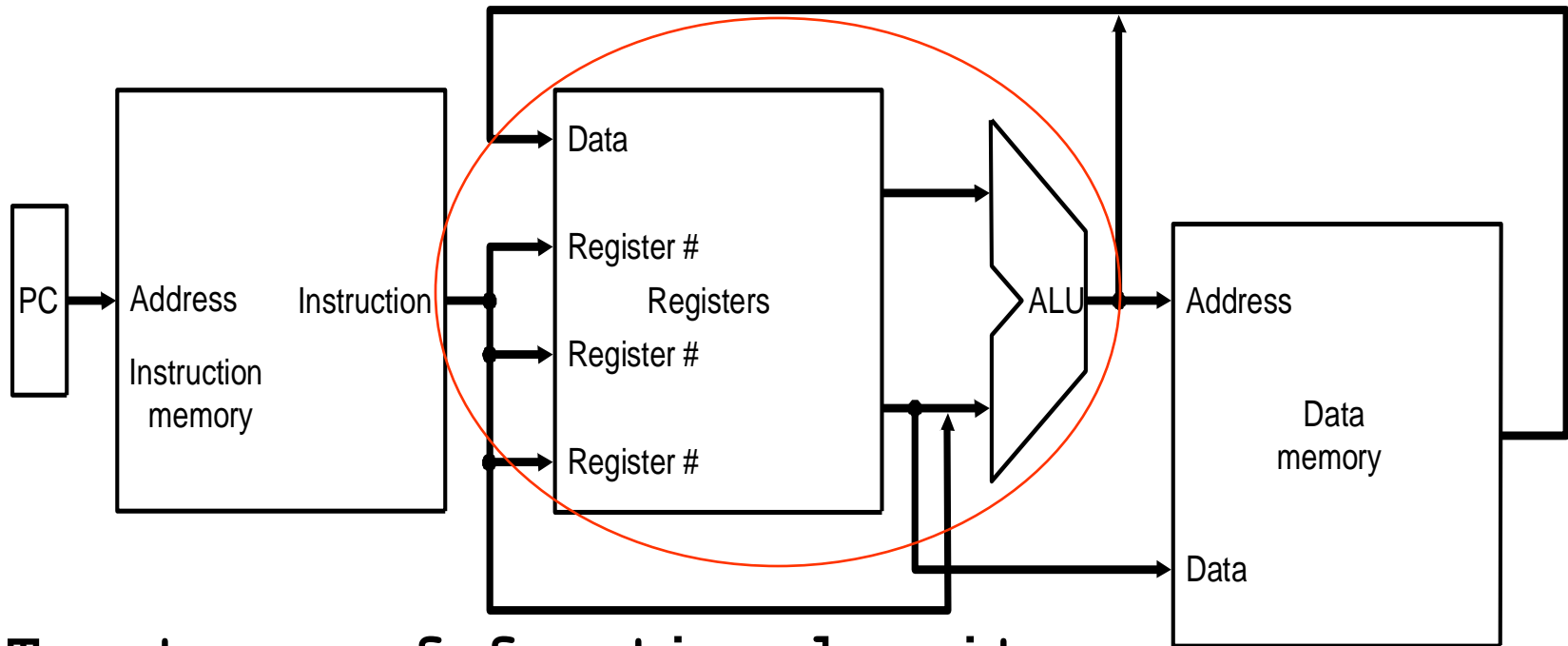


Two types of functional units:

- elements that operate on data values (combinational)
- elements that contain state (sequential)


Register File

■ Built using D flip-flops

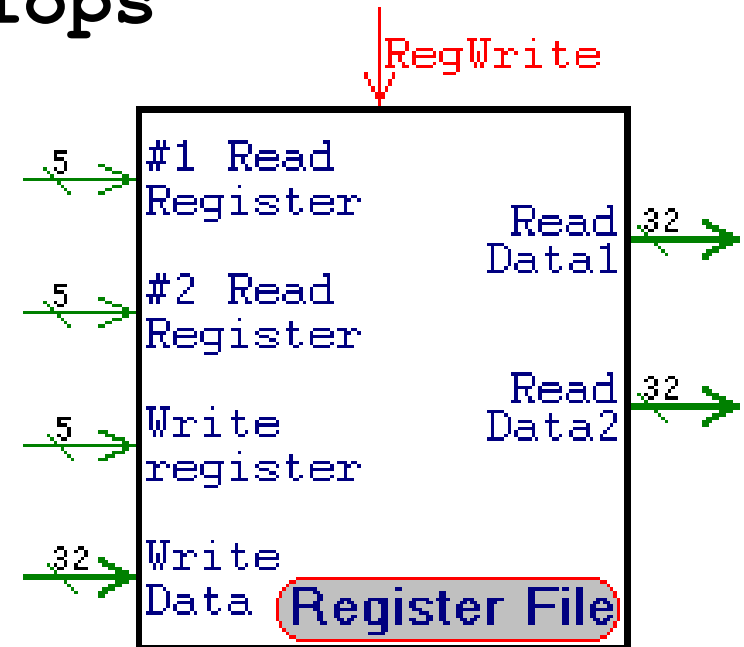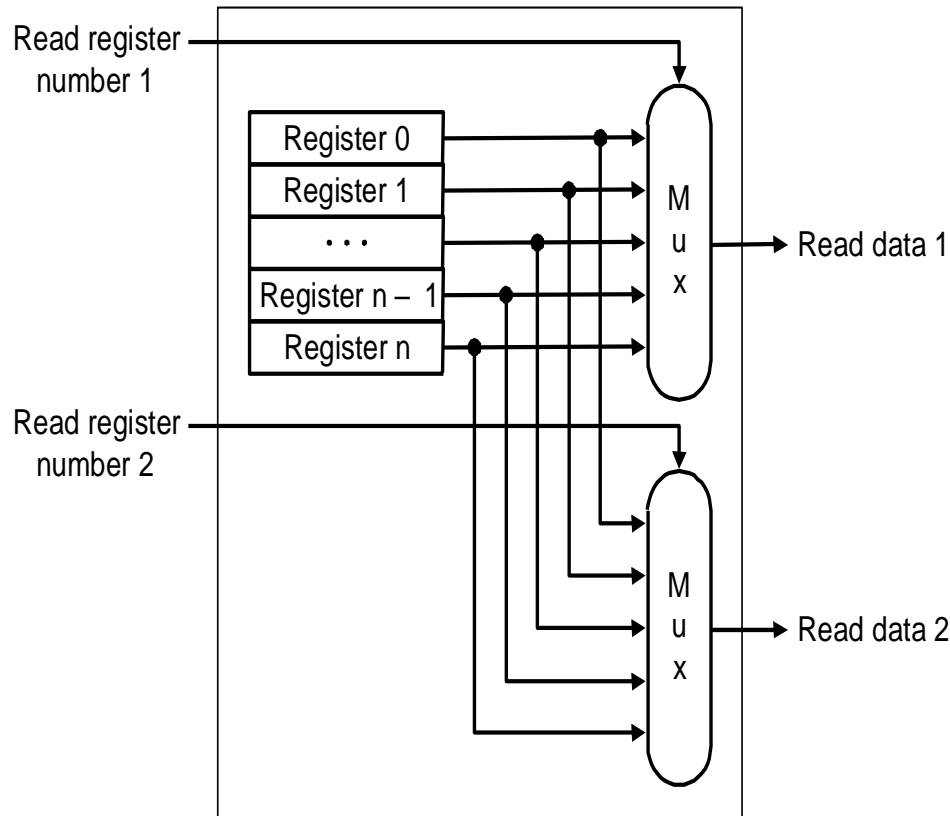

Register File

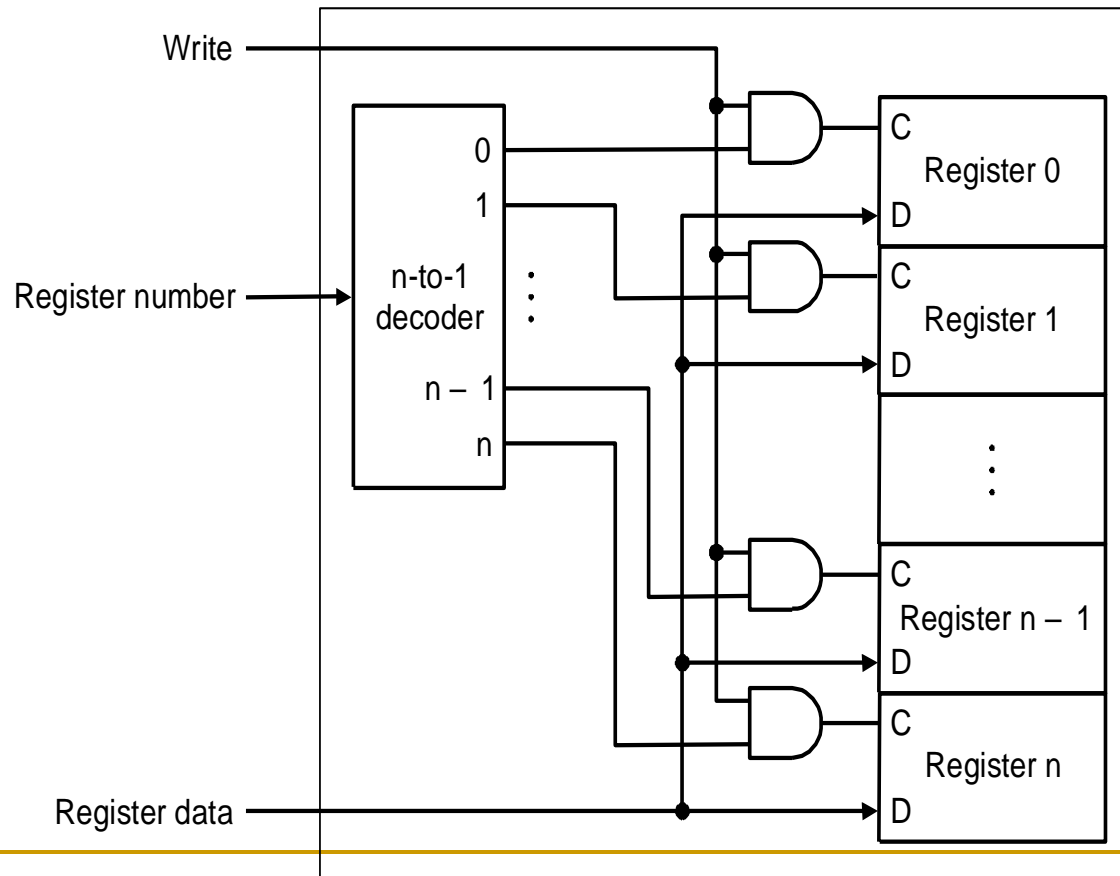
- Note: we still use the real clock to determine when to write



op (6)	rs (5)	rt (5)	rd (5)	shamt	func (6)
--------	--------	--------	--------	-------	----------




Implemente the I type

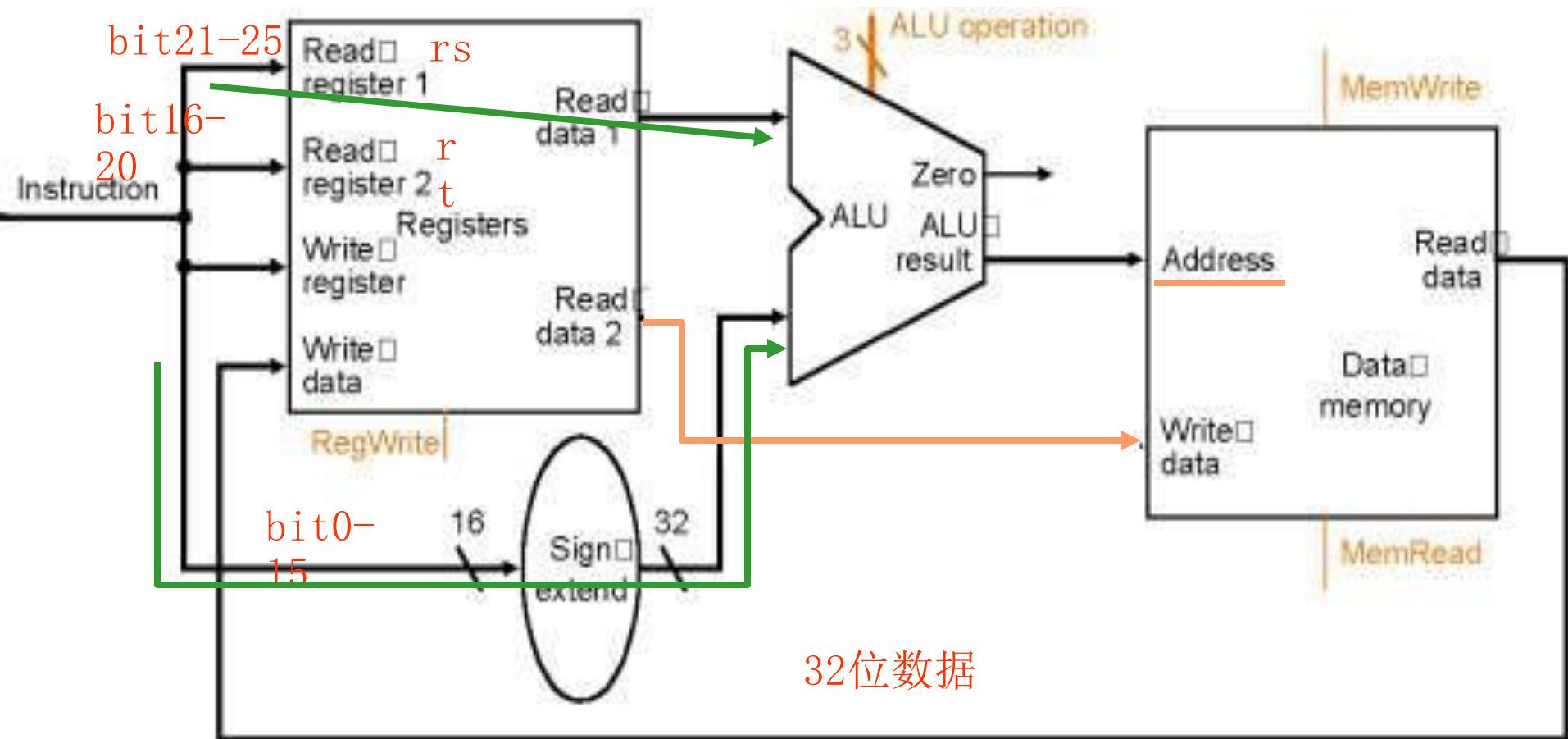


sw \$t0, 200(\$s2)

若\$s2=1000, 则将\$t0存入1200为地址的内存单元的一个字


Implementation of *beq*

 

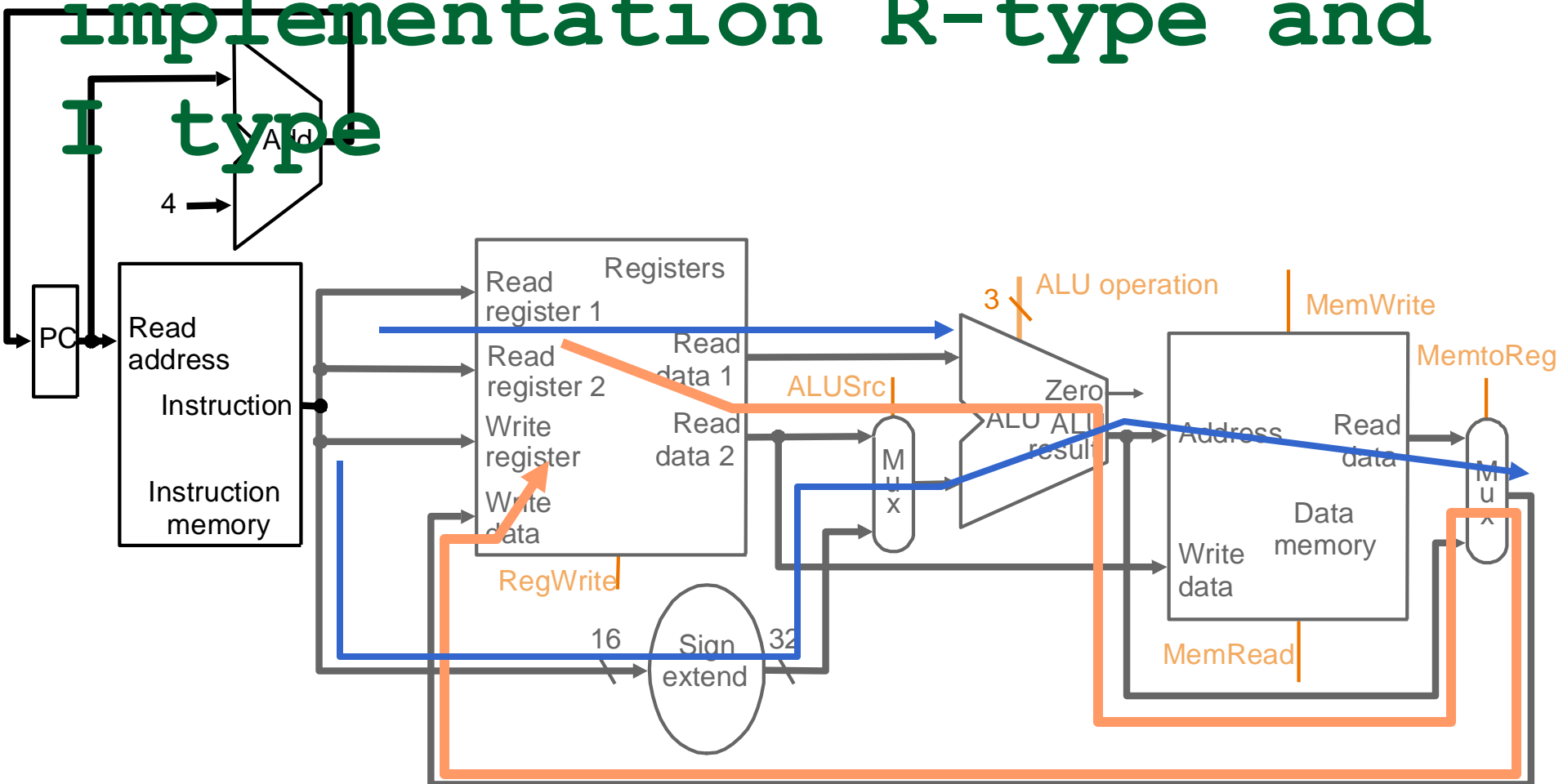
combine the implementation R-type and I type



Implementation of *beq*

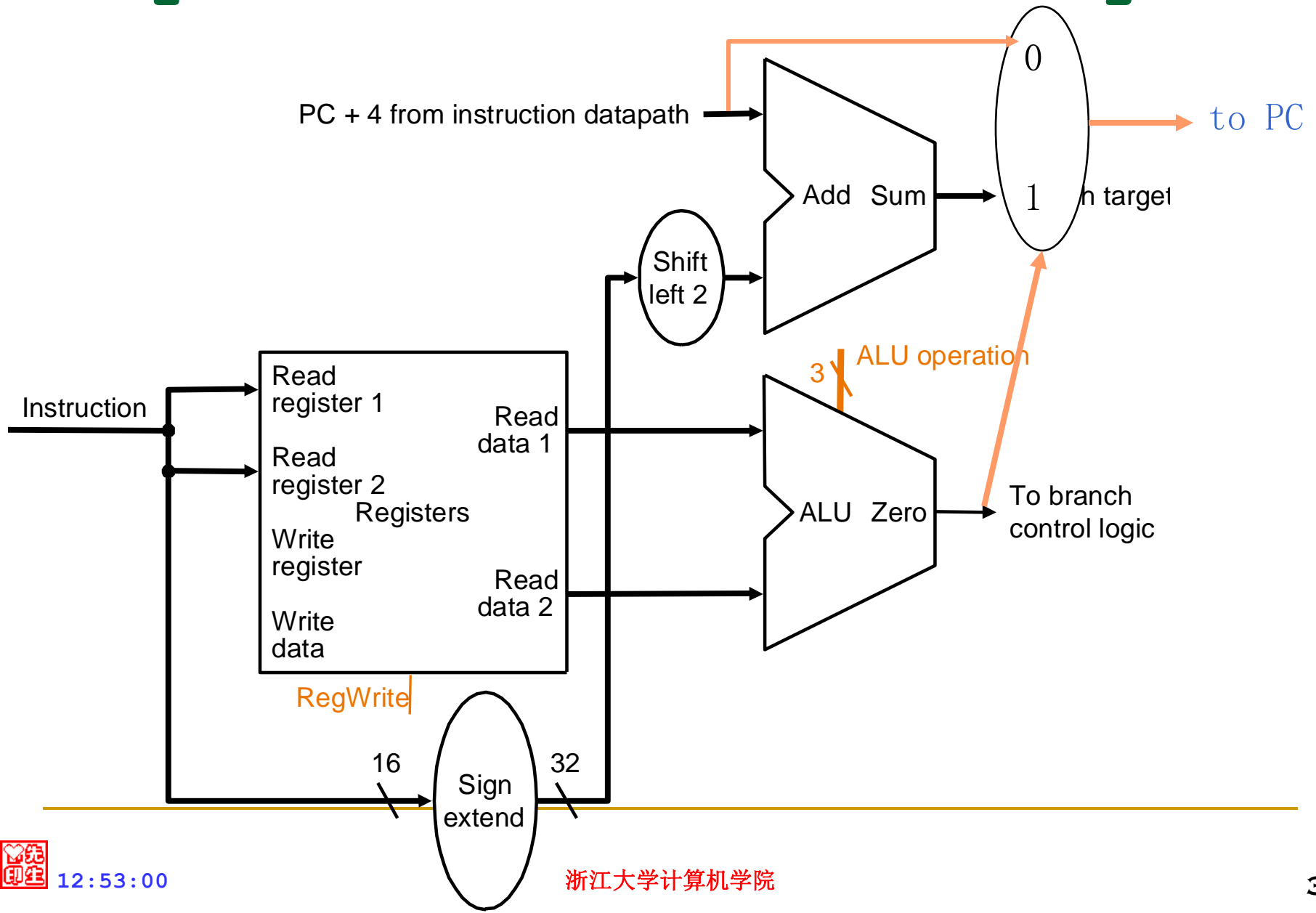


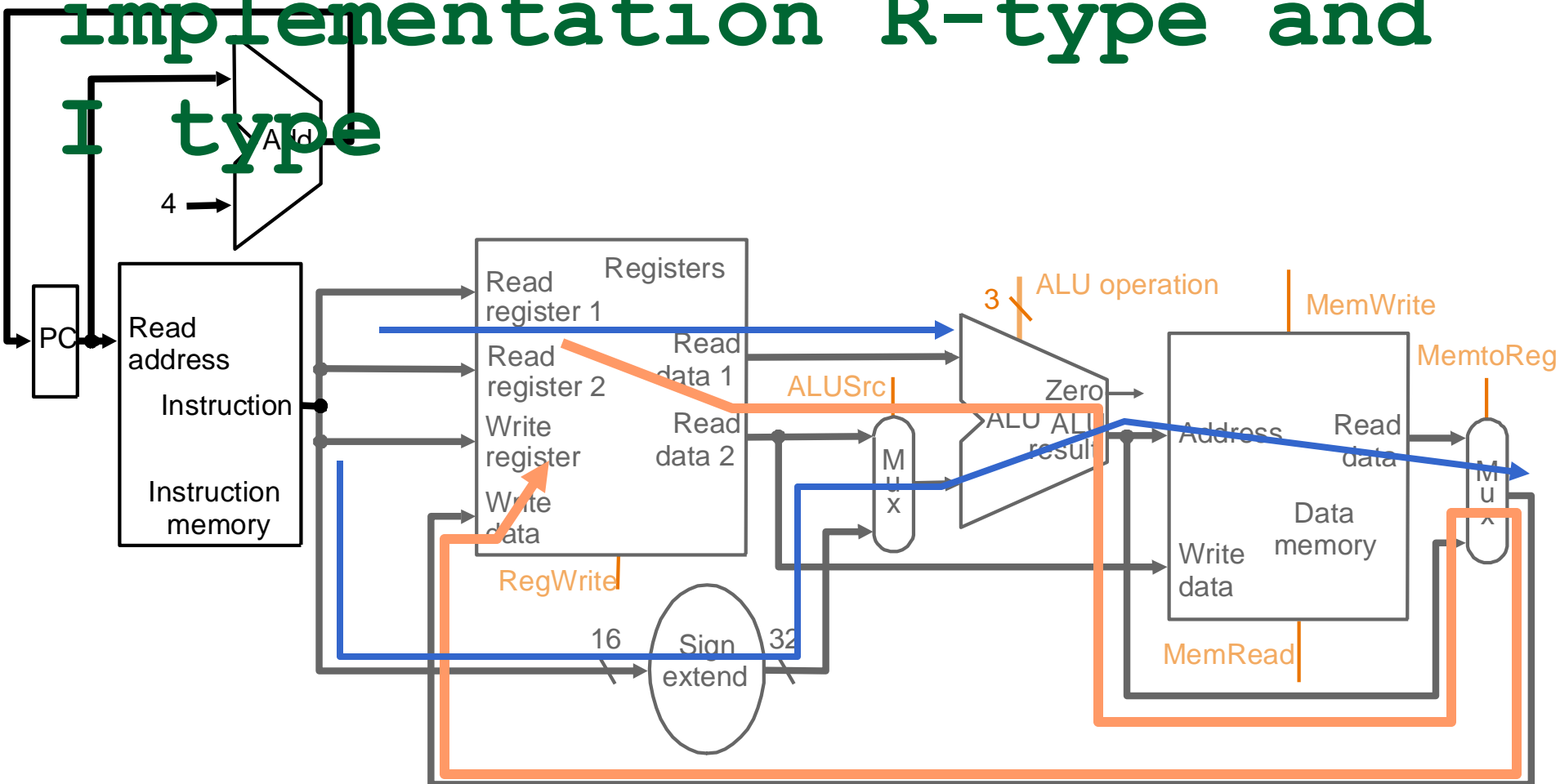combine the implementation R-type and I type



Building the Datapath

 - Use multiplexers to stitch them together



Control

- Selecting the operations to perform (ALU, read/write, etc.)
- Controlling the flow of data (multiplexor inputs)
- Information comes from the 32 bits of the instruction

■ Example:

--	--	--	--	--	--

--	--	--	--	--	--

add \$8, \$17, \$18

Instruction Format:

000000

10001

10010

01000


00000

100000

Control

- e.g., what should the ALU do with this instruction

- Example: `lw $1, 100($2)`

 

op
rs
rt
16 bit offset

ALU control input

000 AND

001 OR

010 add


110 subtract

111 set-on-less-than


Why is the code for subtract 110 and not 011?

The ALU control

instruction format:

 

Bnegate	op	uasge	
0		00	
and			
0		01	or
0		10	+
1		10	-
1		11	
slt			

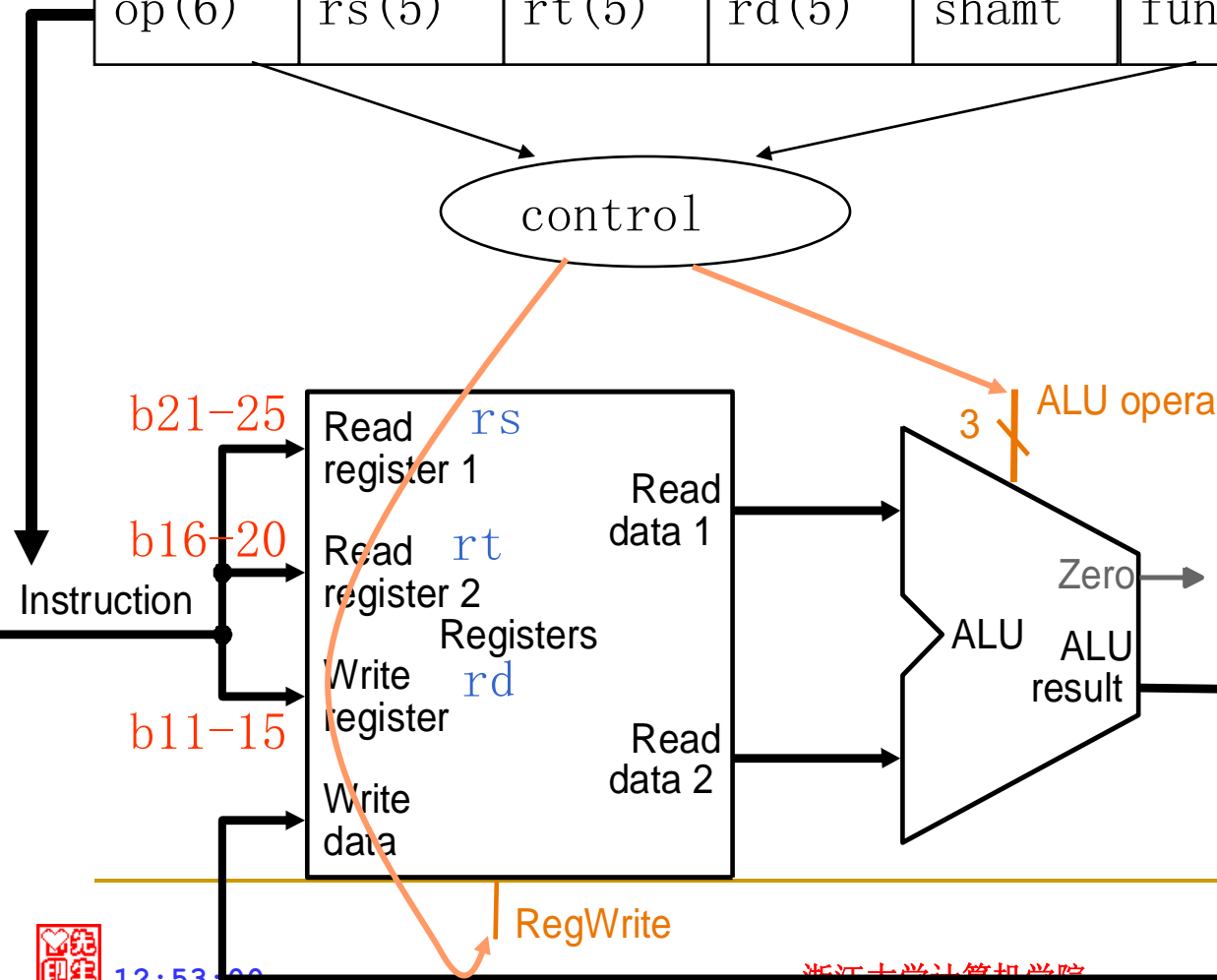

The ALU control


■ 与ALU有关的指令

编码 ALUop

□ **sw / lw** 00

□ **beq** 01

□ **R-type** 10

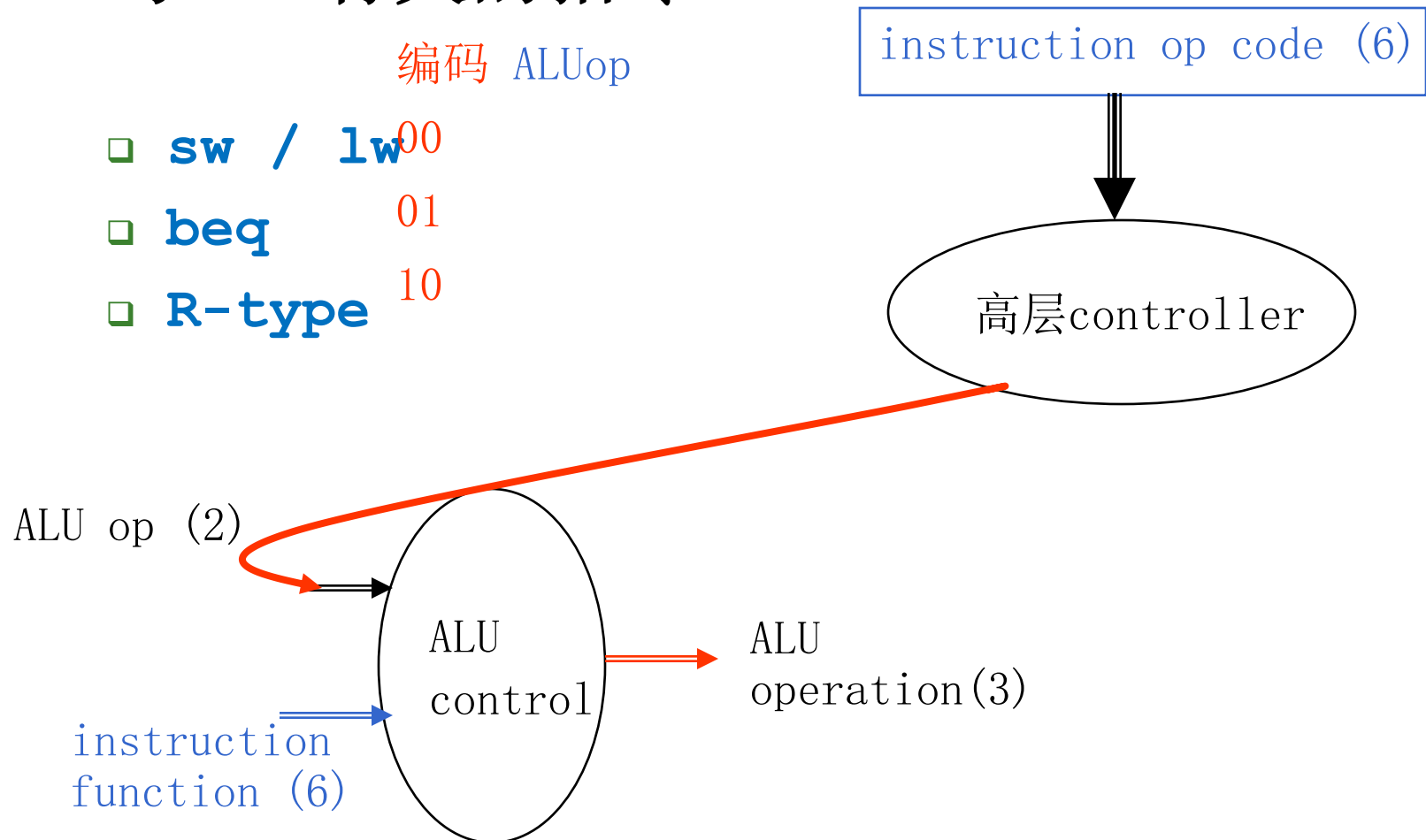

The ALU control

- Must describe hardware to compute 3-bit ALU control input
 - given instruction type
 - 00 = lw, sw
 - 01 = beq,
 - 10 = R-type
 - function code for arithmetic


ALUOp computed from instruction type

- Describe ALUOp into gates


don't care

ALUOp		Funct field						Operation
ALUOp1	ALUOp0	F5	F4	F3	F2	F1	F0	
0	0	X	X	X	X	X	X	010
X	1	X	X	X	X	X	X	110
1	X	X	X	0	0	0	0	010
1	X	X	X	0	0	1	0	110
1	X	X	X	0	1	0	0	000
1	X	X	X	0	1	0	1	001
1	X	X	X	1	0	1	0	111

The ALU control

 



The ALU control

 


Designing the Main Control Unit

 - Main Control Unit function
 - ALU op (2)
 - other control signals (p. 359)
 - 4 Mux
 - 3 R/W



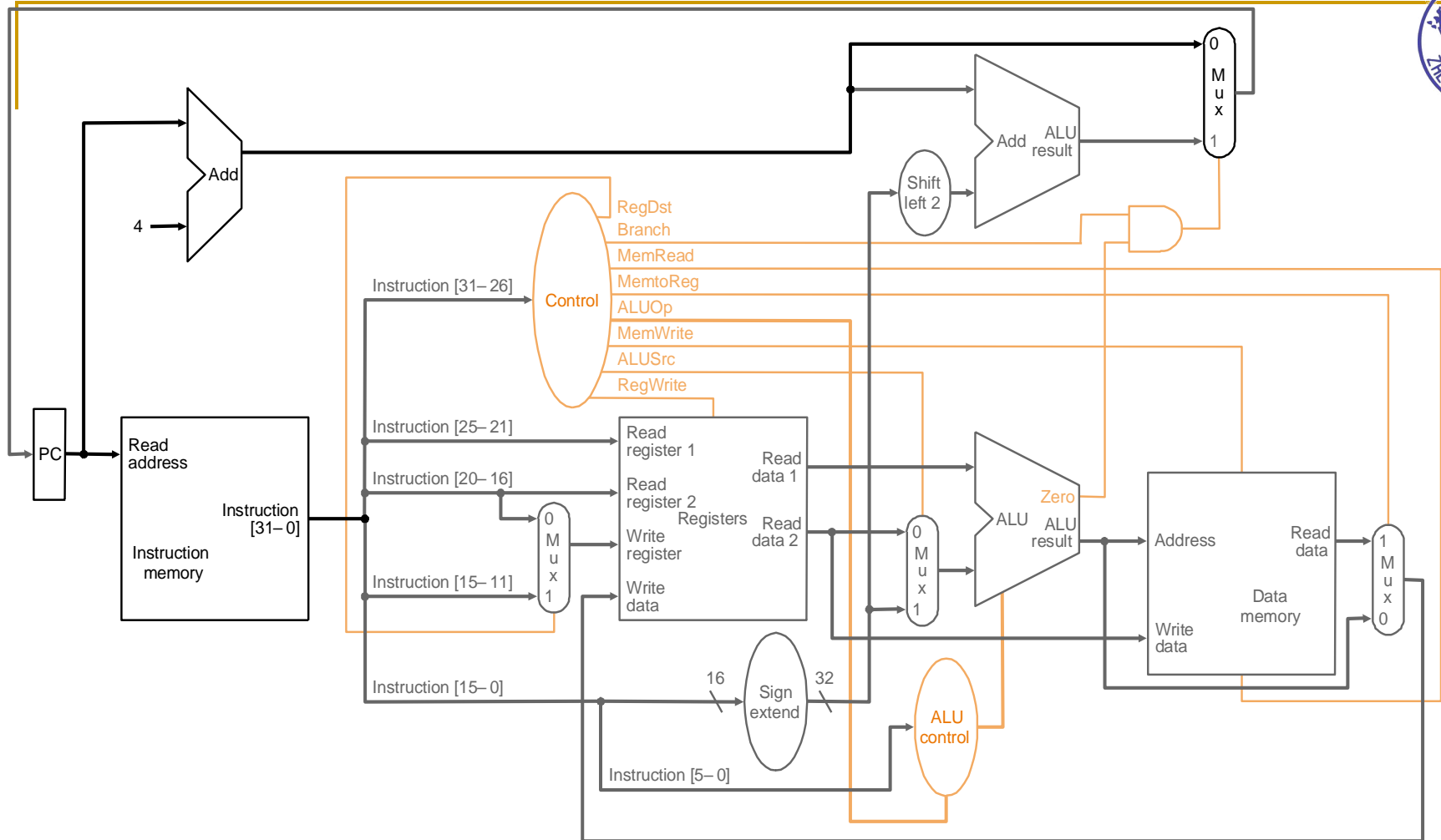

Instruction	RegDst	ALUSrc	Memto-Reg	Reg Write	Mem Read	Mem Write	Branch	ALUOp1	ALUp0
R-format	1	0	0	1	0	0	0	1	0
lw	0	1	1	1	1	0	0	0	0
sw	X	1	X	0	0	1	0	0	0
beq	X	0	X	0	0	0	1	0	1

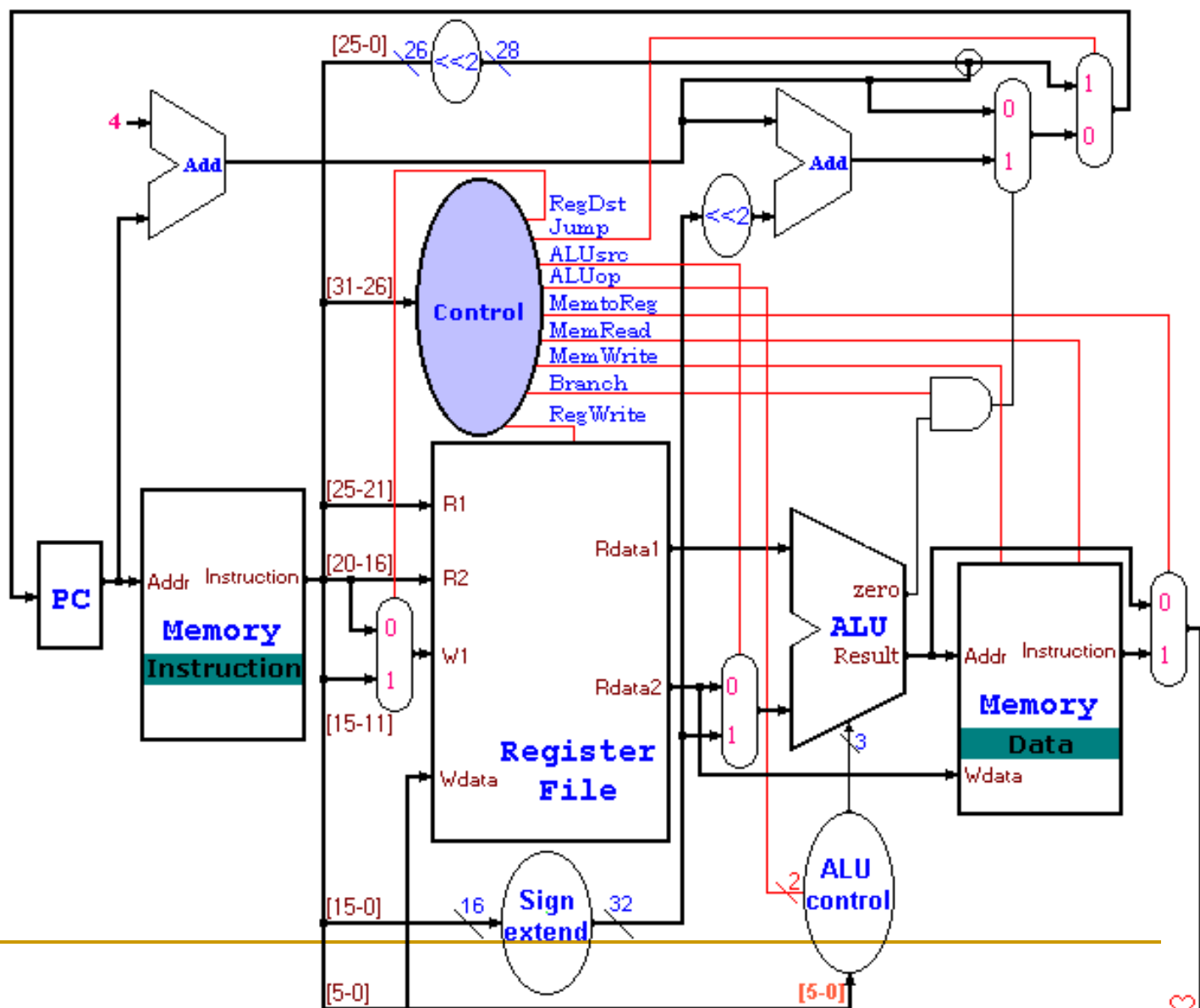

Control


- Simple combinational logic (truth tables)

R-type

lw 35

sw 43


beq 4

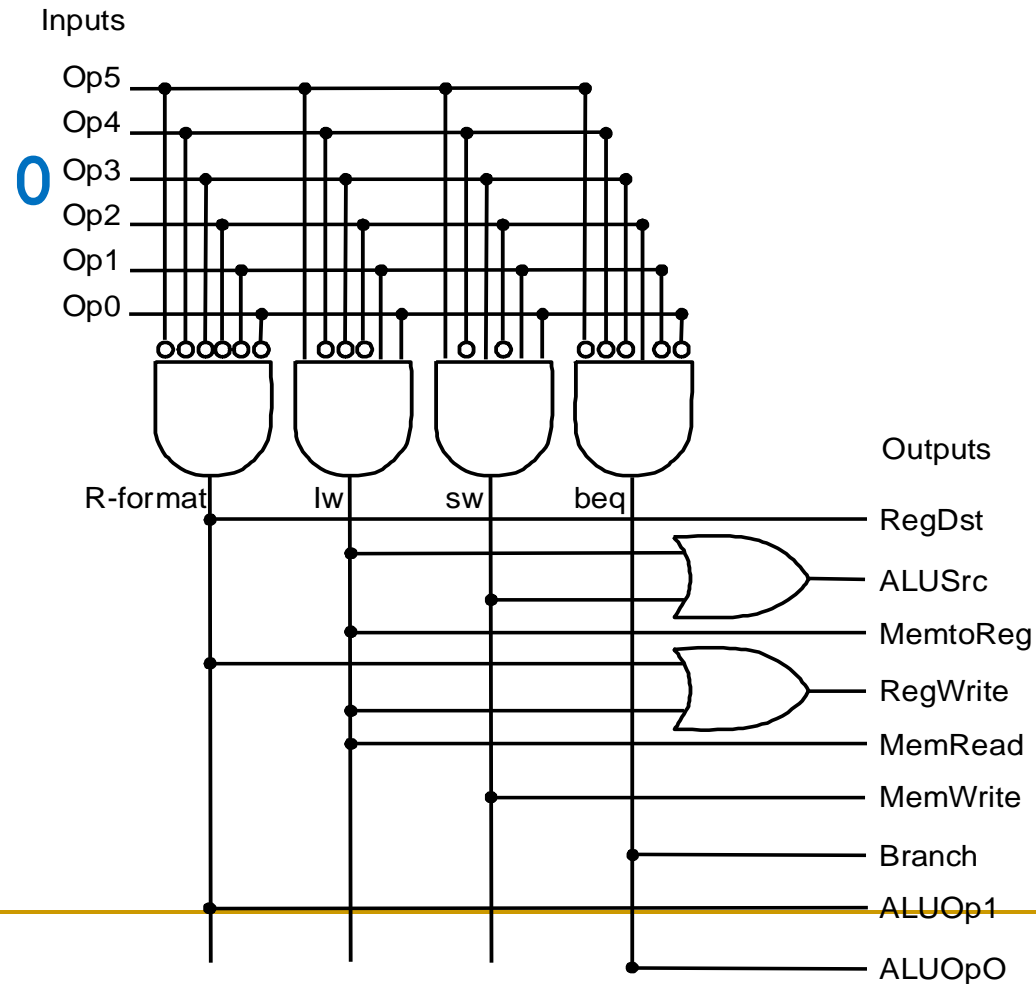

j instruction


■ instruction format

□ j Label

 


■ Implementation
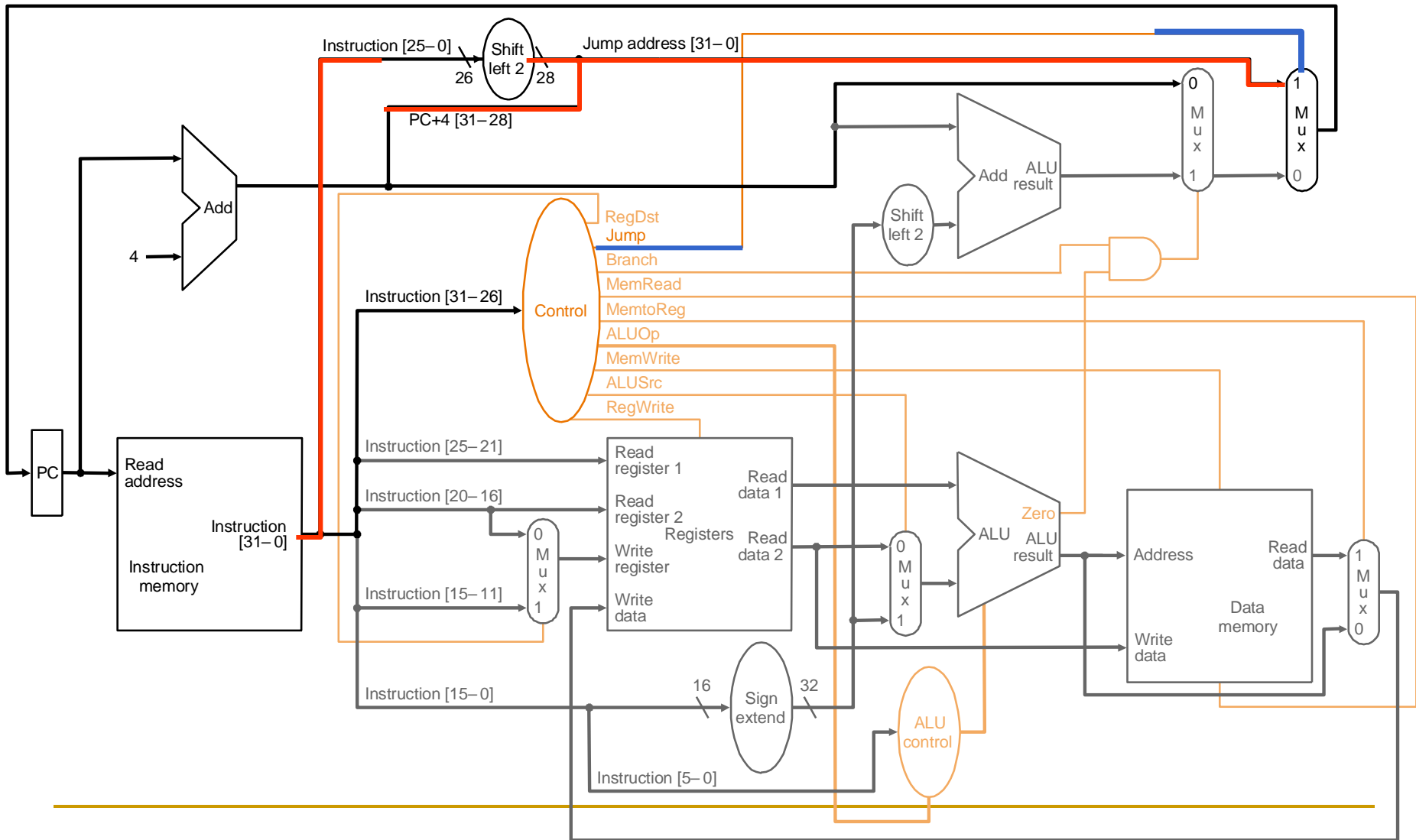
$$\square pc = pc_{28 \sim 31} + \frac{26\text{bits-address}}{4} *$$



Our Simple Control

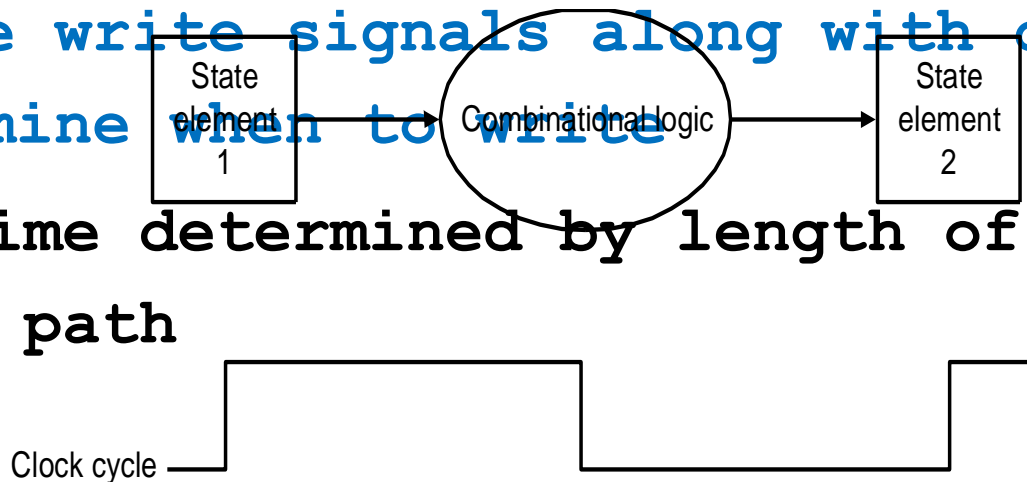- **Structure**
 - All of the logic is combinational
 - We wait for everything to settle down, and the right thing to be done
 - ALU might not produce right answer?right away
 - we use write signals along with clock to determine when to write
- Cycle time determined by length of the longest path




We are ignoring some details like setup and hold times

Single Cycle Implementation

■ Calculate cycle time assuming negligible delays except:

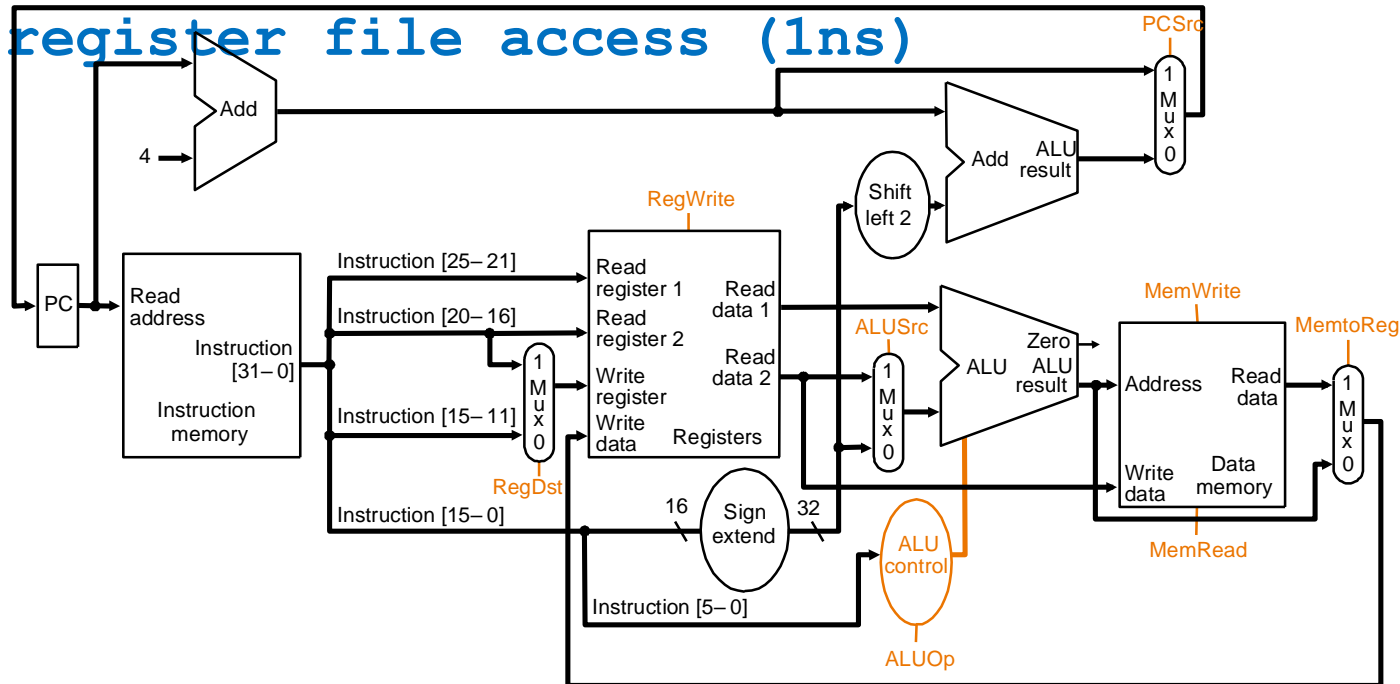□ memory (2ns), ALU and adders (2ns), register file access (1ns)




Where we are headed

■ Single Cycle Problems:


- ❑ what if we had a more complicated instruction like floating point?
- ❑ wasteful of area

■ One Solution:

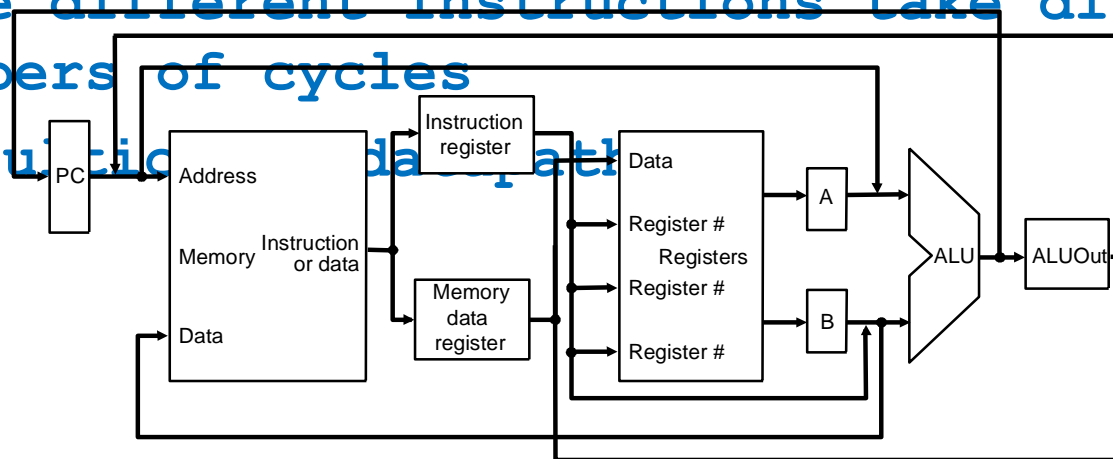
- ❑ use a **pipelined** cycle time
- ❑ have different instructions take different numbers of cycles
- ❑ a **dedicated** data path



Implementation of *beq*

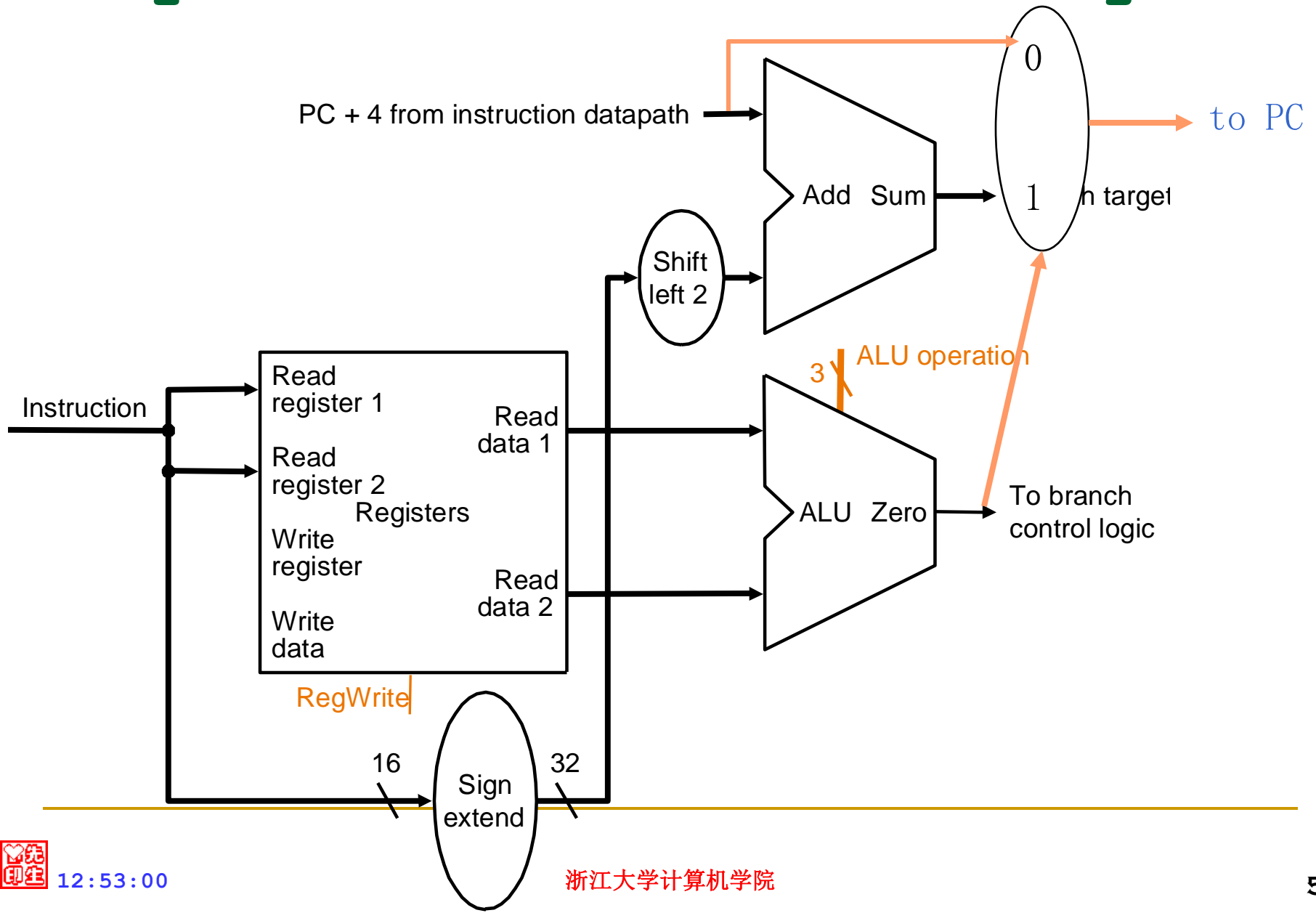


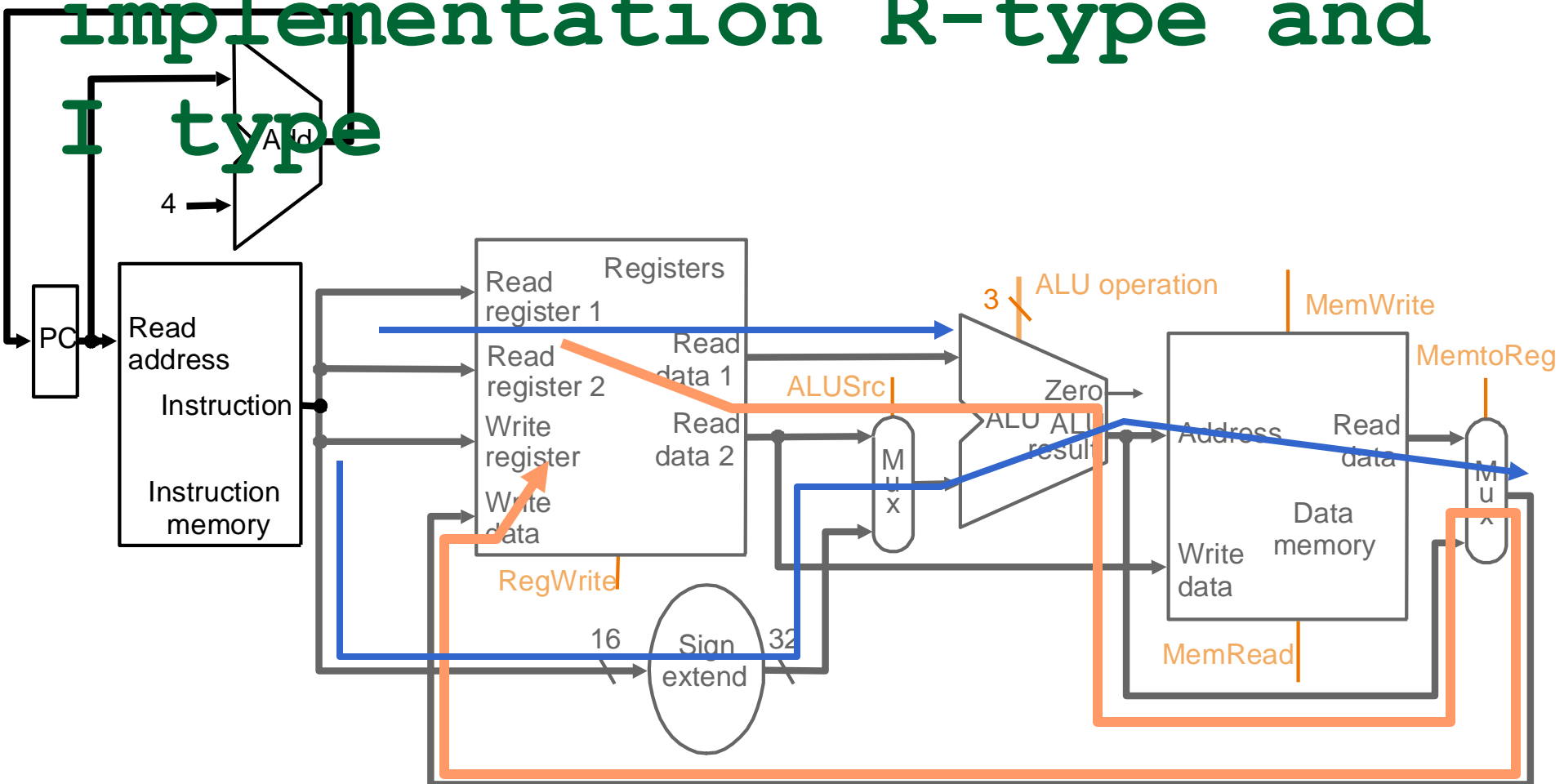combine the implementation R-type and I type



Building the Datapath

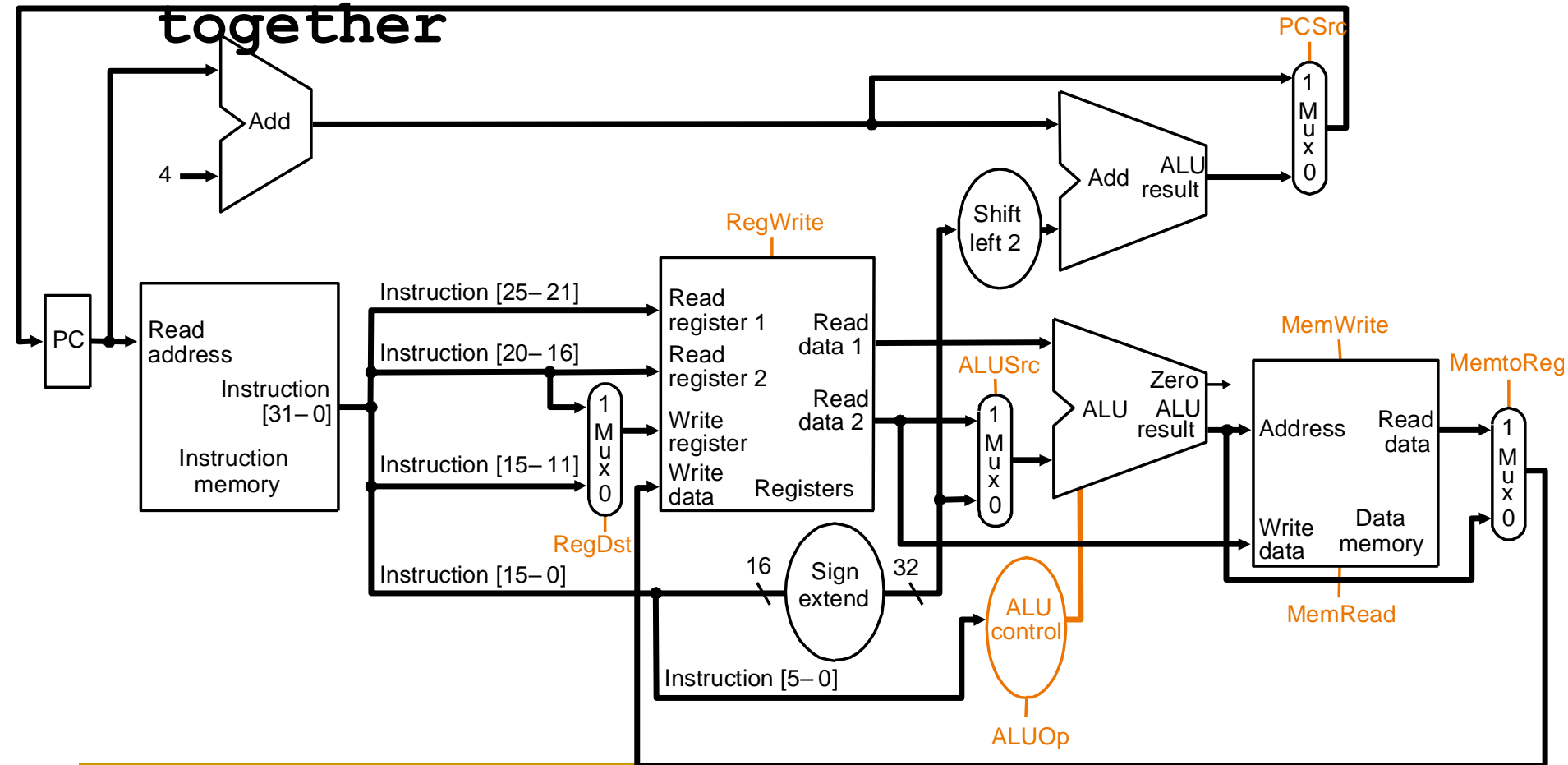- Use multiplexers to stitch them together





Control

- Selecting the operations to perform (ALU, read/write, etc.)
- Controlling the flow of data (multiplexor inputs)
- Information comes from the 32 bits of the instruction




Control

■ Example:

add \$8, \$17, \$18 Instruction Format:

000000 10001 10010 01000
 00000 100000

 


- ALU's operation based on instruction type and function code

Control

- e.g., what should the ALU do with this instruction

- Example: `lw $1, 100($2)`

 

op	rs	rt	16 bit offset
ALU control input			

000 AND

001 OR

010 add



110 subtract

111 set-on-less-than

Why is the code for subtract 110 and not 011?

The ALU control

instruction format:

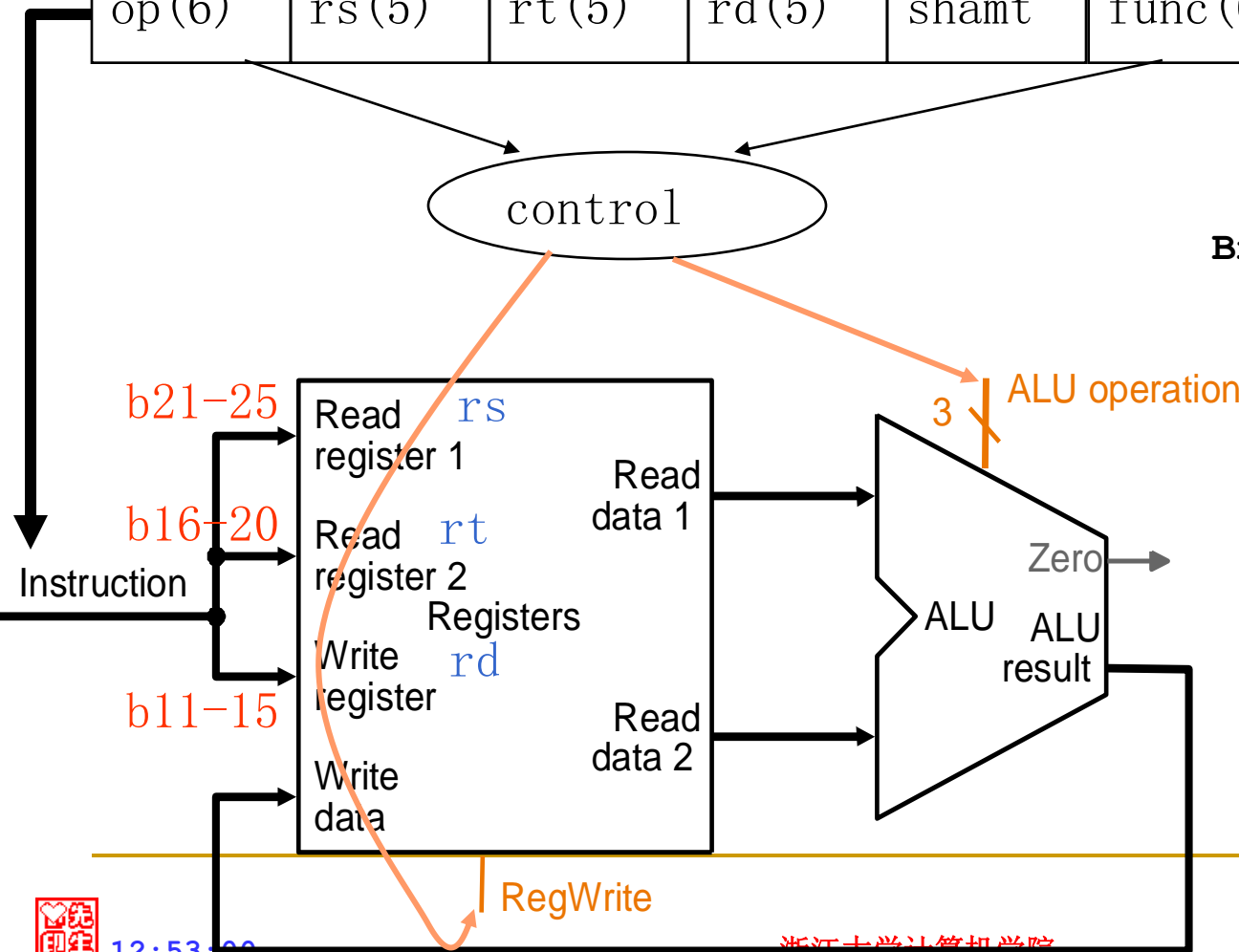 

Bnegate	op	uasge
0		00
and		
0		01
or		
0		10
+		
1		10
-		
1		11
slt		

The ALU control


■ 与ALU有关的指令

编码 ALUop

□ **sw / lw** 00

□ **beq** 01

□ **R-type** 10

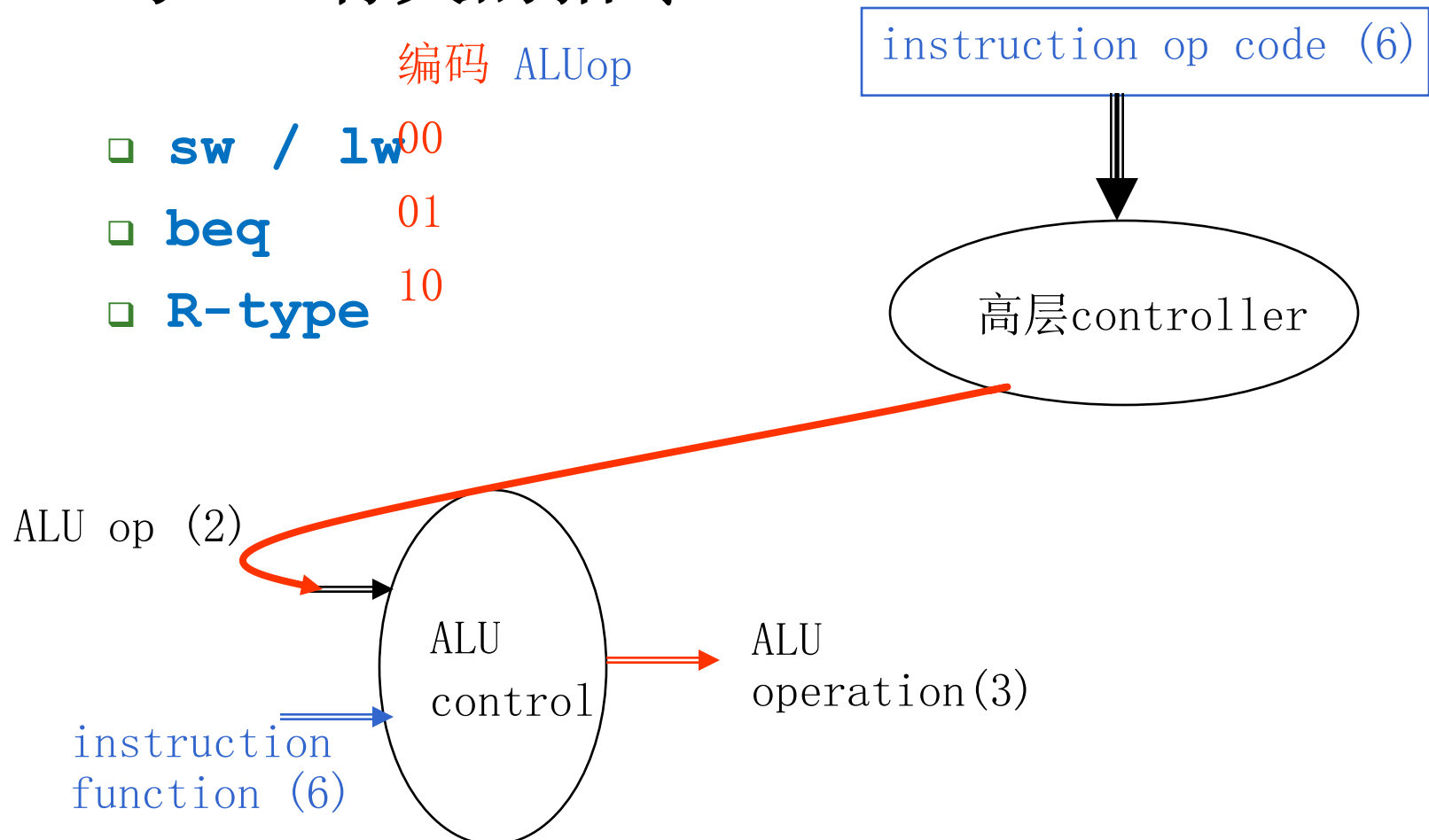

The ALU control

- Must describe hardware to compute 3-bit ALU control input
 - given instruction type
 - 00 = lw, sw
 - 01 = beq,
 - 10 = R-type
 - function code for arithmetic


ALUOp computed from instruction type

- Describe into gates


don't care

ALUOp		Funct field						Operation
ALUOp1	ALUOp0	F5	F4	F3	F2	F1	F0	
0	0	X	X	X	X	X	X	010
X	1	X	X	X	X	X	X	110
1	X	X	X	0	0	0	0	010
1	X	X	X	0	0	1	0	110
1	X	X	X	0	1	0	0	000
1	X	X	X	0	1	0	1	001
1	X	X	X	1	0	1	0	111

The ALU control

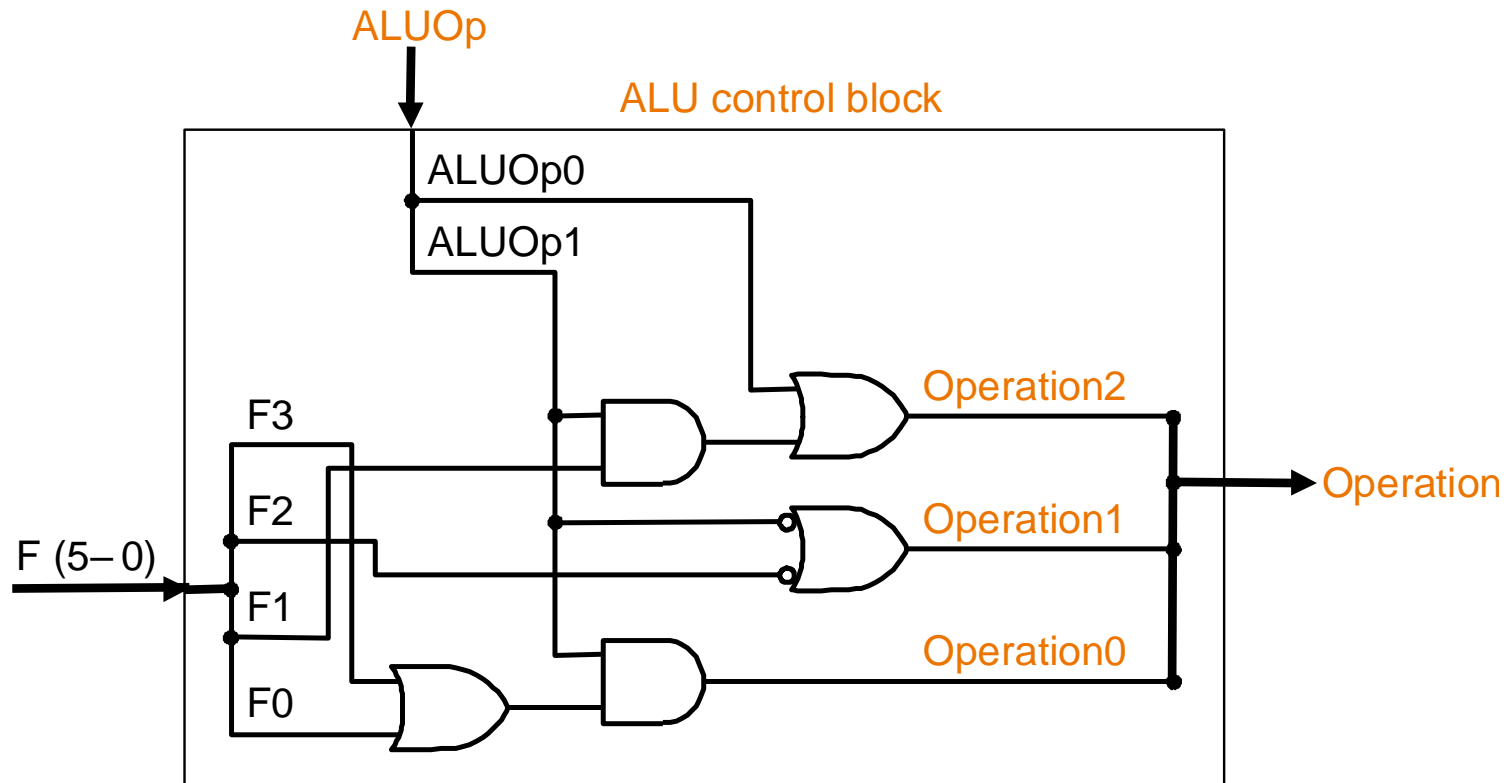



The ALU control

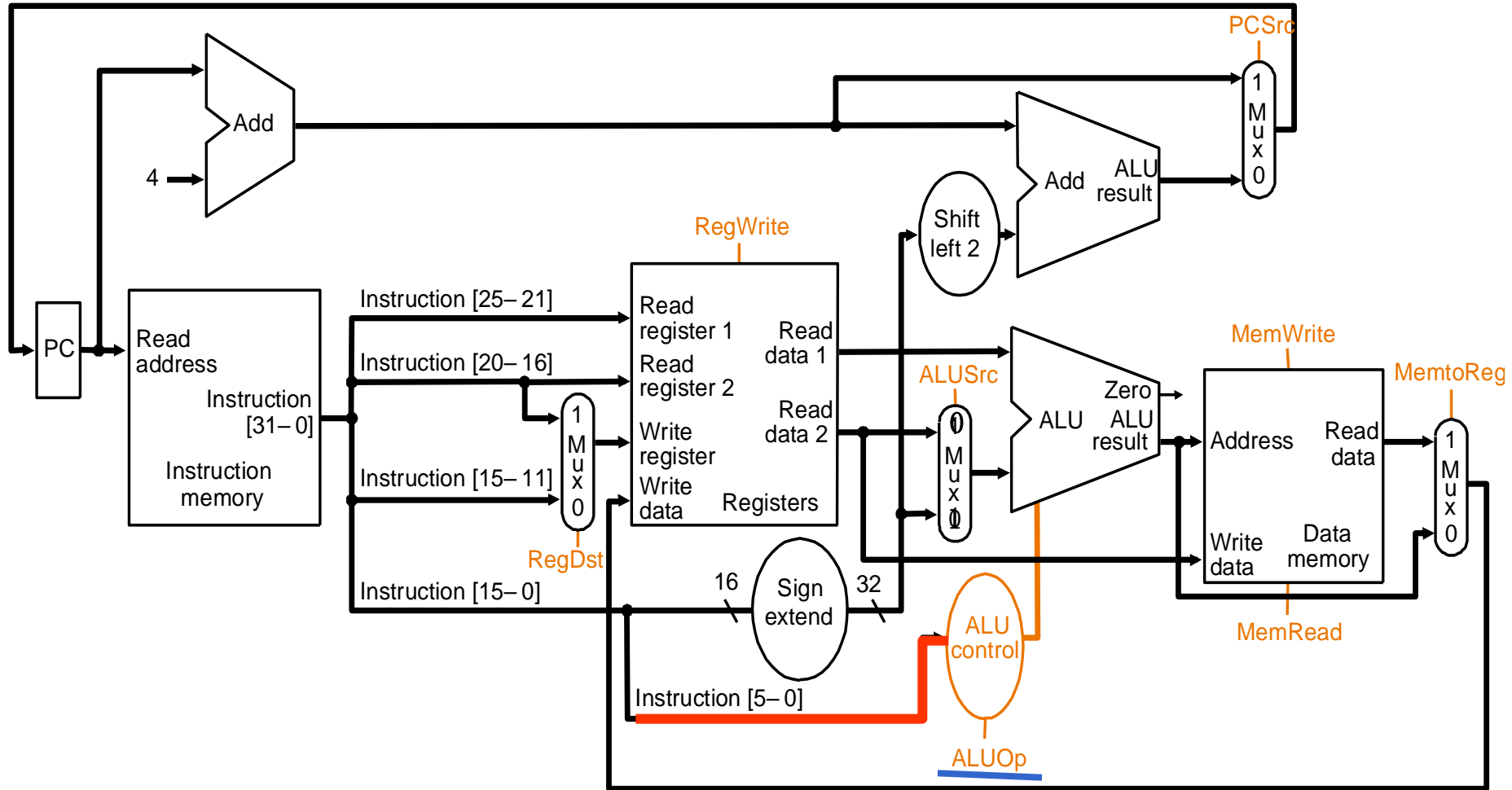

Designing the Main Control Unit

 - Main Control Unit function
 - ALU op (2)
 - other control signals (p. 359)
 - 4 Mux
 - 3 R/W



 

Instruction	RegDst	ALUSrc	Memto-Reg	Reg Write	Mem Read	Mem Write	Branch	ALUOp1	ALUp0
R-format	1	0	0	1	0	0	0	1	0
lw	0	1	1	1	1	0	0	0	0
sw	X	1	X	0	0	1	0	0	0
beq	X	0	X	0	0	0	1	0	1

Control


- Simple combinational logic (truth tables)

R-type

lw 35

sw 43


beq 4

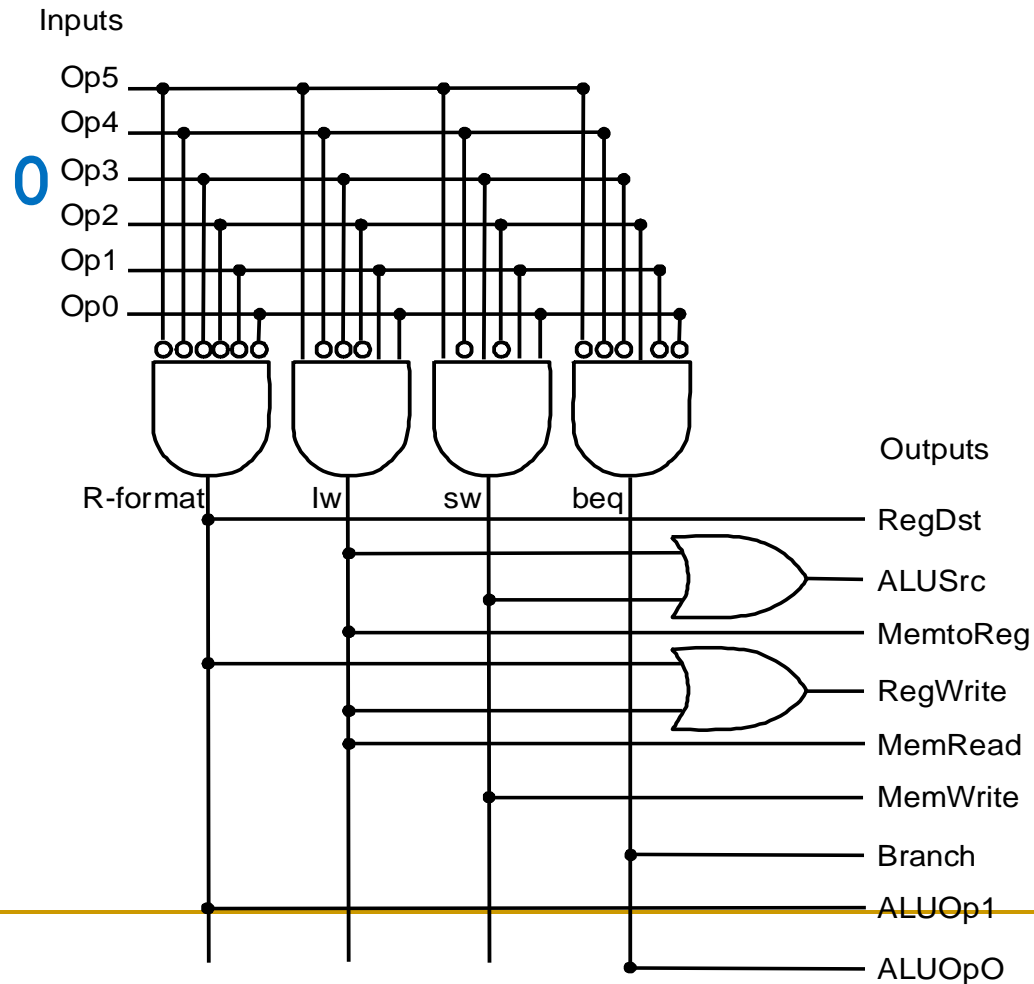

j instruction


■ instruction format

□ j Label

 

■ Implementation
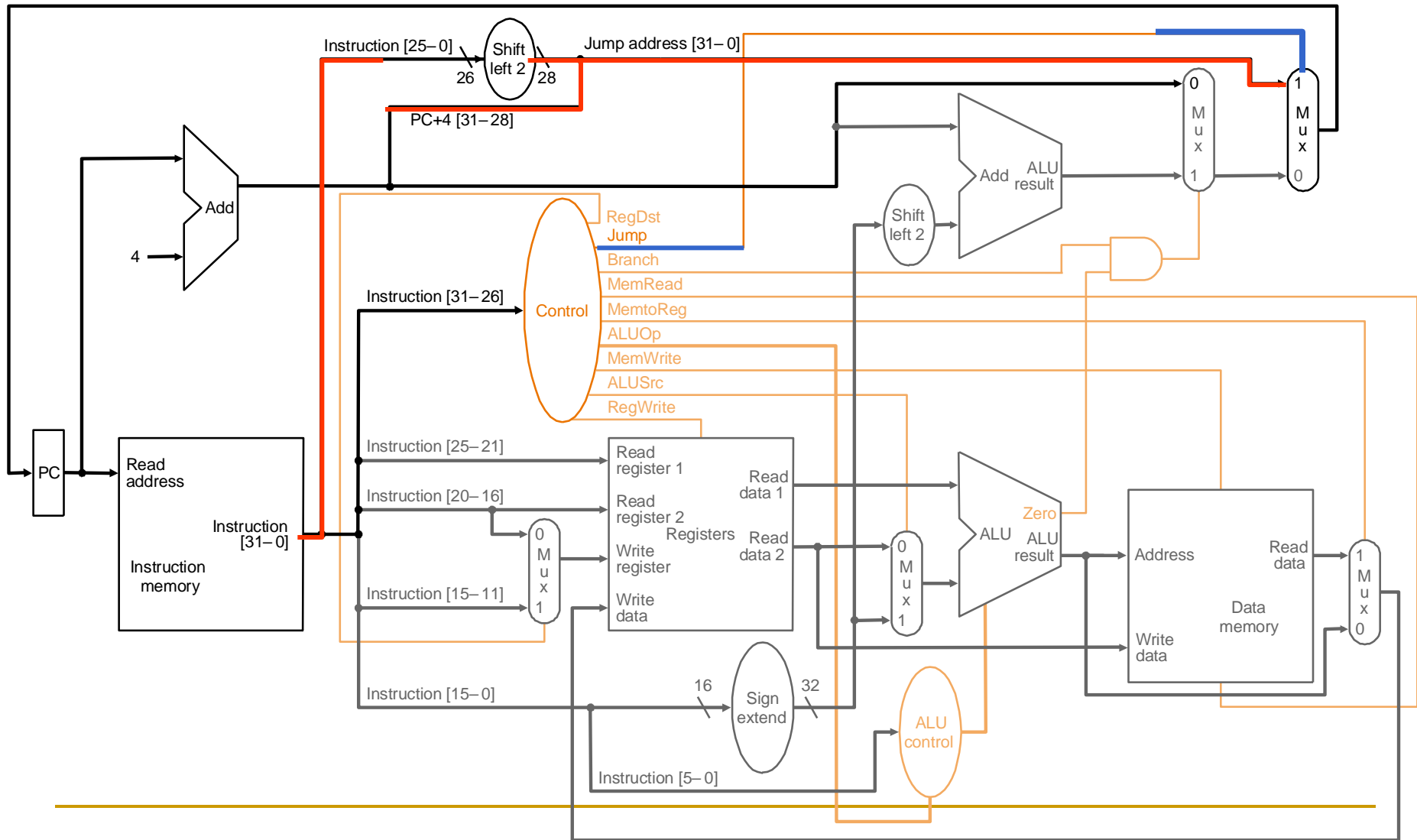
$$\square pc = pc_{28 \sim 31} + \frac{26\text{bits-address}}{4} *$$



Our Simple Control

Structure

- All of the logic is combinational
- We wait for everything to settle down, and the right thing to be done
 - ALU might not produce right answer? right away
 - we use write signals along with clock to determine when to write

- Cycle time determined by length of the longest path




We are ignoring some details like setup and hold times

Single Cycle Implementation

■ Calculate cycle time assuming negligible delays except:

 □ memory (2ns), ALU and adders (2ns), register file access (1ns)




Where we are headed

- Single Cycle Problems:
 - what if we had a more complicated instruction like floating point?
 - wasteful of area
- One Solution:
 - use a smaller cycle time
 - have different instructions take different numbers of cycles

Multicycle Approach

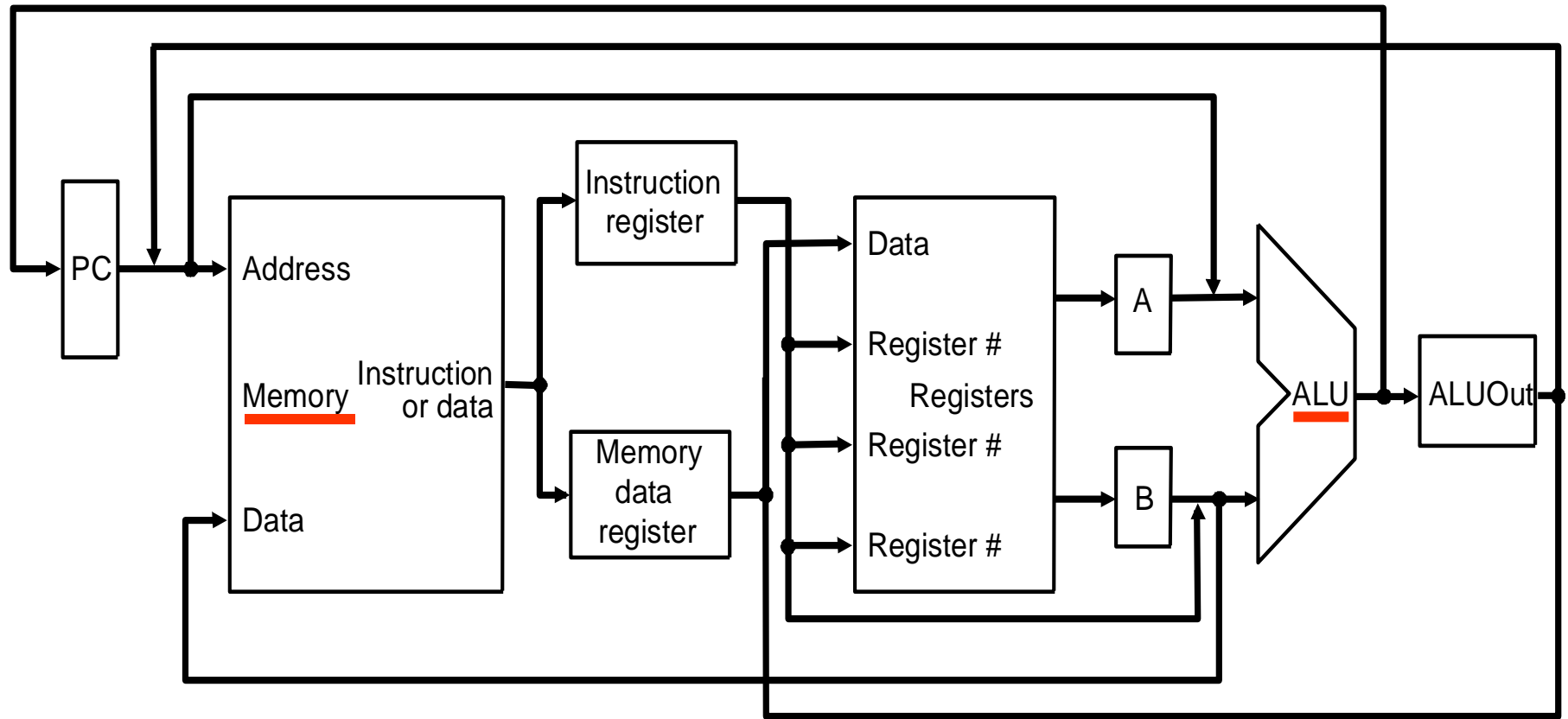
- We will be reusing functional units
 - ALU used to compute address and to increment PC
 - Memory used for instruction and data
- Our control signals will not be determined solely by instruction
 - e.g., what should the ALU do for a subtract instruction?
- We will use a finite state machine for control



Review: finite state machines

■ Finite state machines:

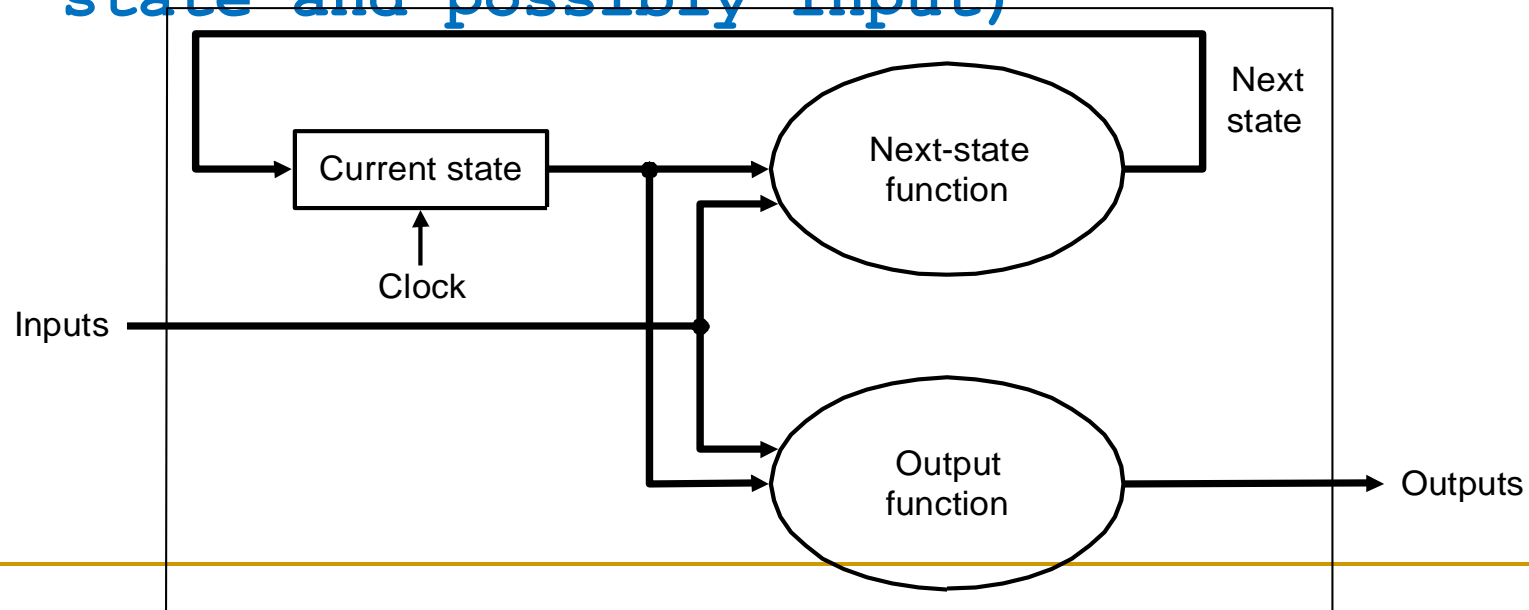- a set of states
- next state function (determined by current state and the input)
- output function (determined by current state and possibly input)





Multicycle Approach

- Break up the instructions into steps, each step takes a cycle
 - balance the amount of work to be done
 - restrict each cycle to use only one major functional unit
- At the end of a cycle
 - store values for use in later cycles (easiest thing to do)
 - introduce additional internal registers

The diagram illustrates the flow of instructions and data in a computer system. The PC (Program Counter) provides the address for the Memory and the value for the ALU. The Memory block outputs data to the Memory data register. The Instruction register and Memory data register are highlighted with red boxes. The ALU has two inputs, A and B, which are also highlighted with red boxes. The ALU output is ALUOut. Red arrows point to the Memory Data register, the ALU input B, and the ALU output.

先生印

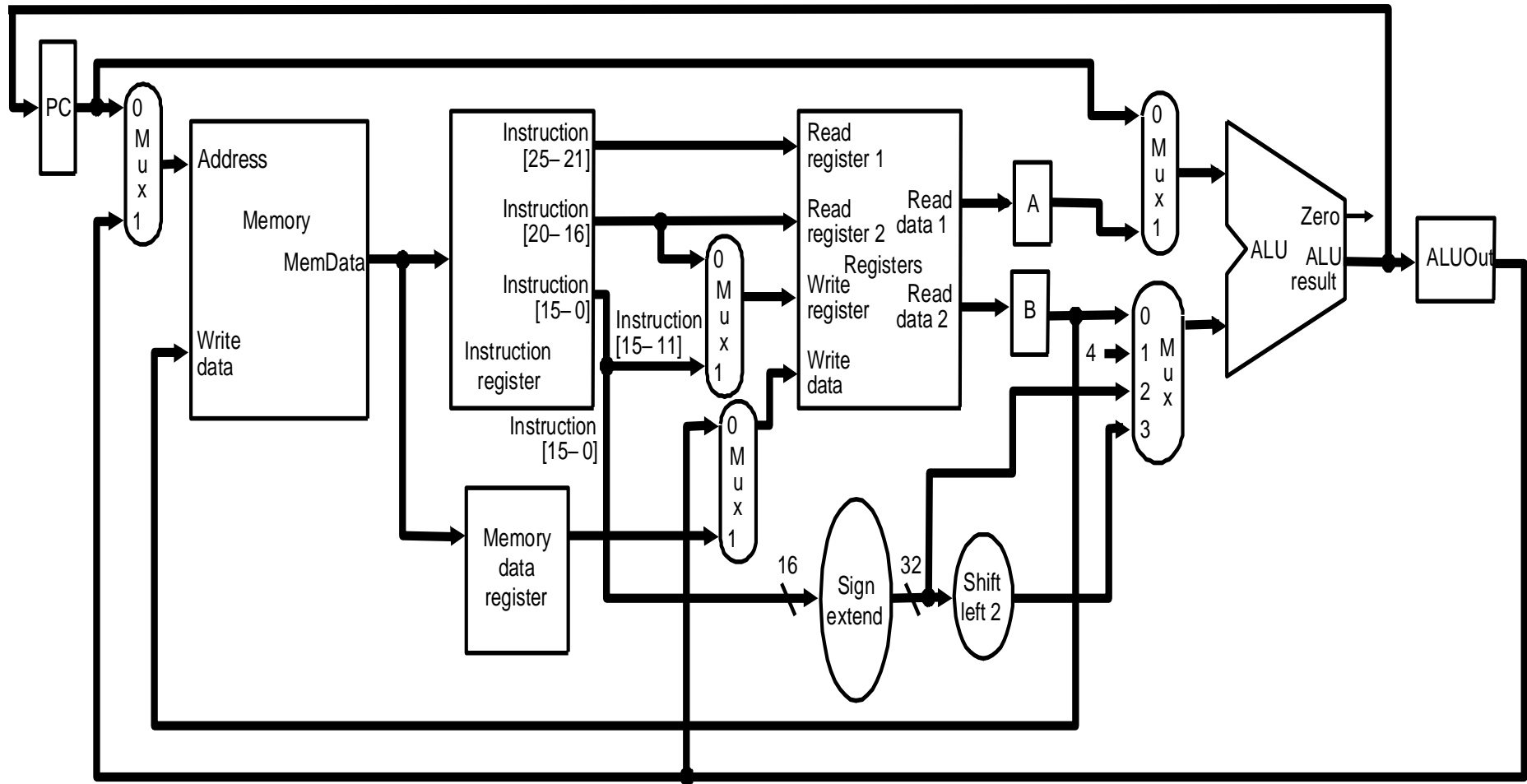

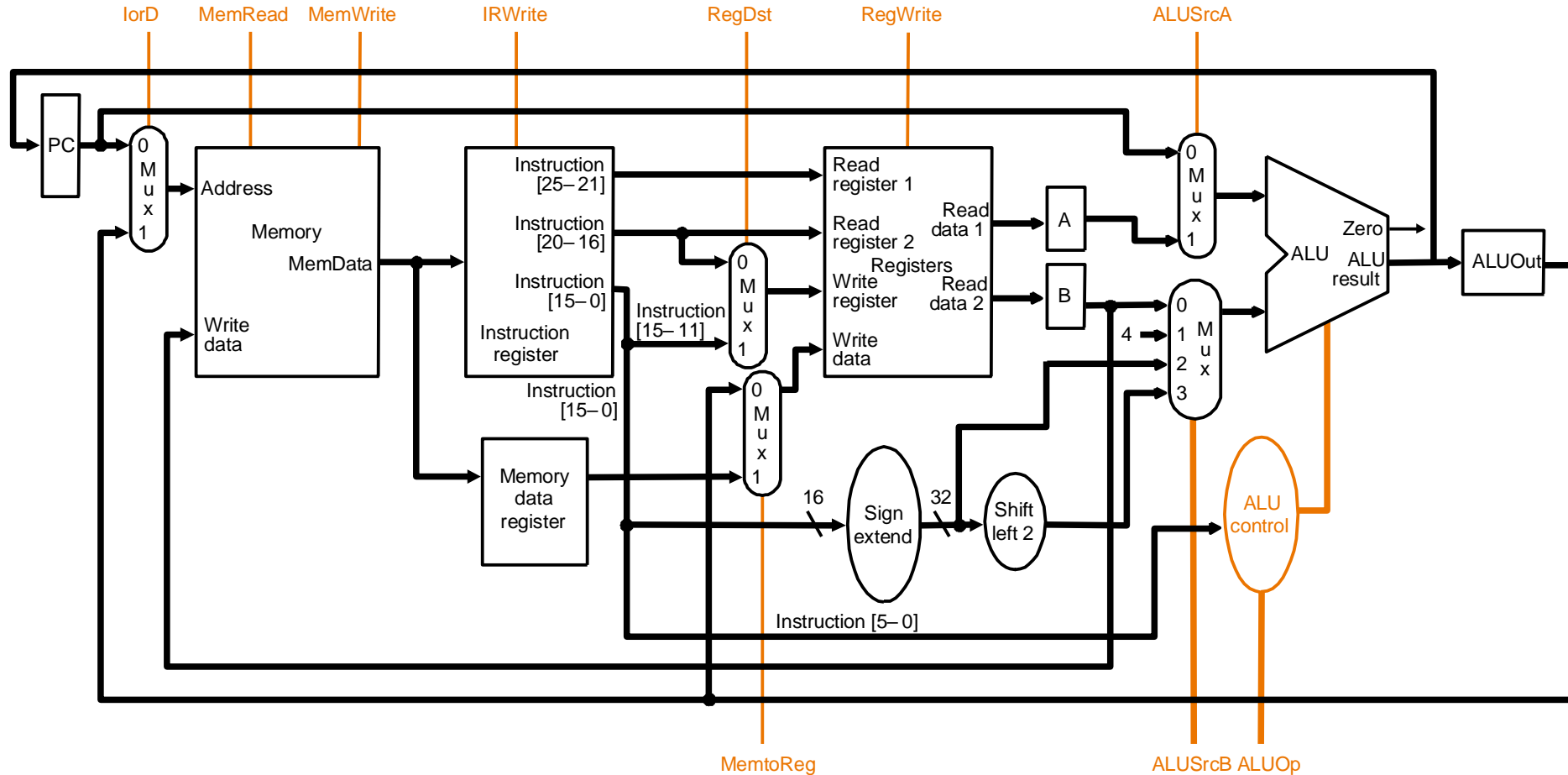

■ PC 的改变方式

□ **seq:** $pc = pc + 4$


□ **beq:** $pc = pc + offset * 4$

□ **j** : $pc = pc_{31-28} + IR_{25-0} \ll 2$

seq: $pc = pc + 4$

beq: $pc = pc + offset * 4$

j : $pc = pc_{31-28} + IR_{25-0} \ll 2$

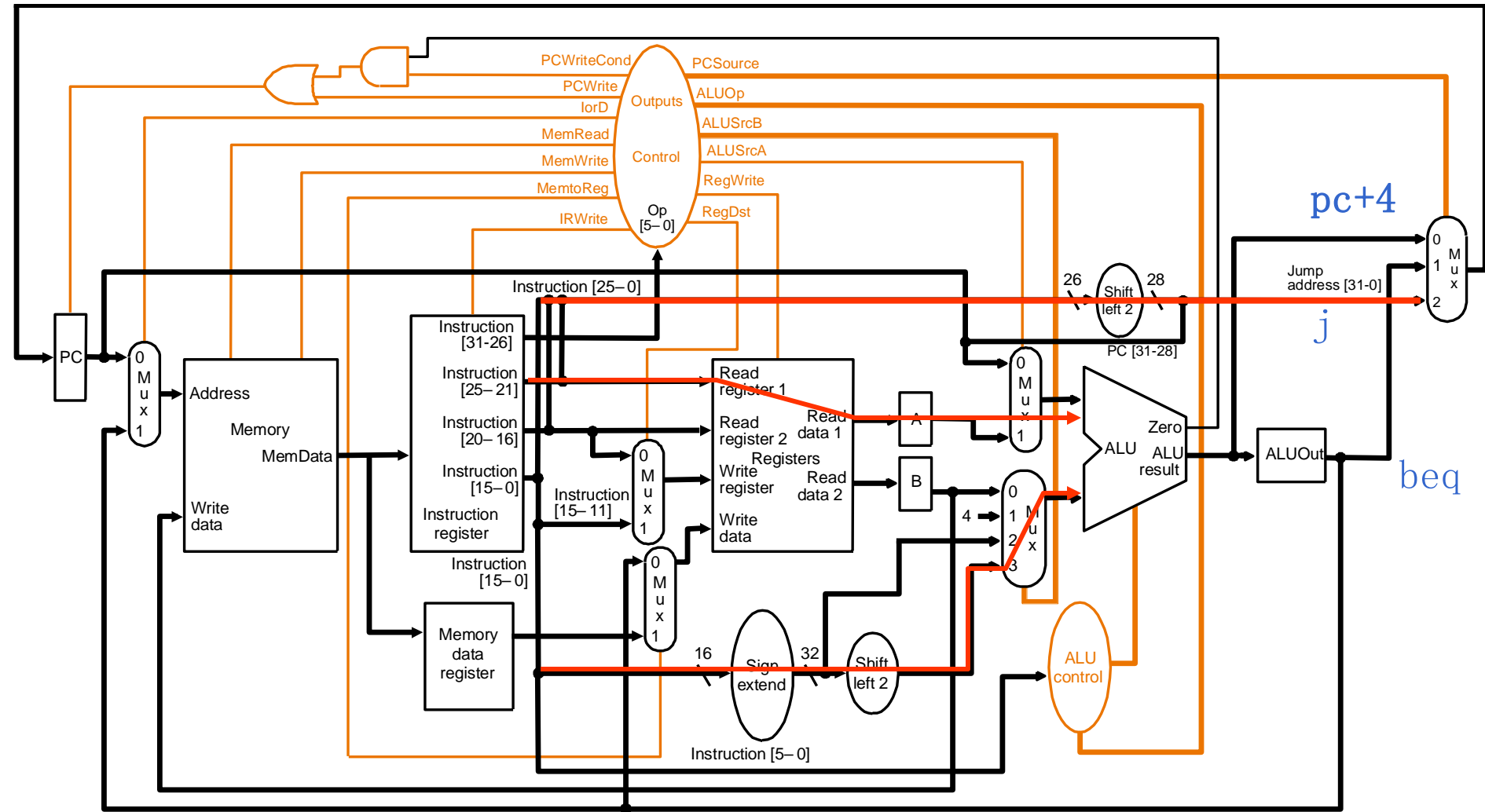



Five Execution Steps

- Instruction Fetch
- Instruction Decode and Register Fetch
- Execution, Memory Address Computation, or Branch Completion
- Memory Access or R-type instruction completion
- Write-back step

INSTRUCTIONS TAKE FROM 3 - 5 CYCLES!



Step 1: Instruction

Fetch

- Use PC to get instruction and put it in the Instruction Register.
- Increment the PC by 4 and put the result back in the PC.
- Can be described succinctly using RTL "Register-Transfer Language"

$IR = Memory[PC];$

$PC = PC + 4;$

Can we figure out the values of the control signals?

What is the advantage of updating the PC now?



Step 2: Instruction

Decode and Register Fetch

- Read registers `rs` and `rt` in case we need them
- Compute the branch address in case the instruction is a branch
- RTL:
$$A = \text{Reg}[\text{IR}[25-21]];$$
$$B = \text{Reg}[\text{IR}[20-16]];$$
$$\text{ALUOut} = \text{PC} + (\text{sign-extend}(\text{IR}[15-0]) \ll 2);$$

We aren't setting any control lines based on the instruction type

(we are busy "decoding" it in our control logic)



Step 3 (instruction dependent)

- ALU is performing one of three functions, based on instruction type
- Memory Reference (lw / sw):
$$\text{ALUOut} = A + \text{sign-extend}(\text{IR}[15-0]);$$
- R-type:
$$\text{ALUOut} = A \text{ op } B;$$

Branch:
$$\text{if } (A == B) \text{ PC} = \text{ALUOut};$$
- jump:
$$\text{pc} = \text{pc}_{31-28} + \text{IR}_{25-0} \ll 2$$



Step 4 (R-type or memory access)

- Loads and stores access memory

$\text{MDR} = \text{Memory}[\text{ALUOut}] ;$

or

$\text{Memory}[\text{ALUOut}] = B ;$

- R-type instructions finish

$\text{Reg}[\text{IR}[15-11]] = \text{ALUOut} ;$

The write actually takes place at the end of the cycle on the edge



Write-back step (step 5)



- `lw`

- `Reg[IR[20-16]] = MDR;`

What about all the other instructions?

Summary :

Step name	Action for R-type instructions	Action for memory-reference instructions	Action for branches	Action for jumps
Instruction fetch	$IR = \text{Memory}[PC]$ $PC = PC + 4$			
Instruction decode/register fetch	$A = \text{Reg} [IR[25-21]]$ $B = \text{Reg} [IR[20-16]]$ $ALUOut = PC + (\text{sign-extend} (IR[15-0]) \ll 2)$			
Execution, address computation, branch/ jump completion	$ALUOut = A \text{ op } B$	$ALUOut = A + \text{sign-extend} (IR[15-0])$	if $(A == B)$ then $PC = ALUOut$	$PC = PC [31-28] \parallel (IR[25-0] \ll 2)$
Memory access or R-type completion	$\text{Reg} [IR[15-11]] = ALUOut$	Load: $MDR = \text{Memory}[ALUOut]$ or Store: $\text{Memory} [ALUOut] = B$		
Memory read completion		Load: $\text{Reg}[IR[20-16]] = MDR$		

Simple Questions

- How many cycles will it take to execute this code?

```
lw $t2, 0($t3)
lw $t3, 4($t3) ←
beq $t2, $t3, Label #assume not
add $t5, $t2, $t3
sw $t5, 8($t3)
```

Label: ...

What is going on during the 8th cycle of execution?

- In what cycle does the actual addition of \$t2 and \$t3 takes place?

Implementing the Control



- Value of control signals is dependent upon:
 - what instruction is being executed
 - which step is being performed
- Use the information were accumulated to specify a finite state machine
 - specify the finite state machine graphically, or
 - use microprogramming
- Implementation can be derived from ~~specification~~





Computer Organization & Design

第02章：MIPS Instruction Set

楼学庆

<http://10.214.47.99/>

[Email:hzlou@163.com](mailto:hzlou@163.com)



玉泉校区曹光彪东楼507室



12:53:00

浙江大学计算机学院



信息安全与技术

第05章：网络攻击技术

§ 5.1：网络攻击概述



玉泉校区曹光彪东楼507室



12:53:00

浙江大学计算机学院



信息安全与技术

第05章：网络攻击技术

§：本章小结



玉泉校区曹光彪东楼507室



12:53:00

浙江大学计算机学院



信息安全与技术

第05章：网络攻击技术

§：思考题



玉泉校区曹光彪东楼507室



12:53:00

浙江大学计算机学院



Thank You!

非常天空

浙江大学计算机学院

